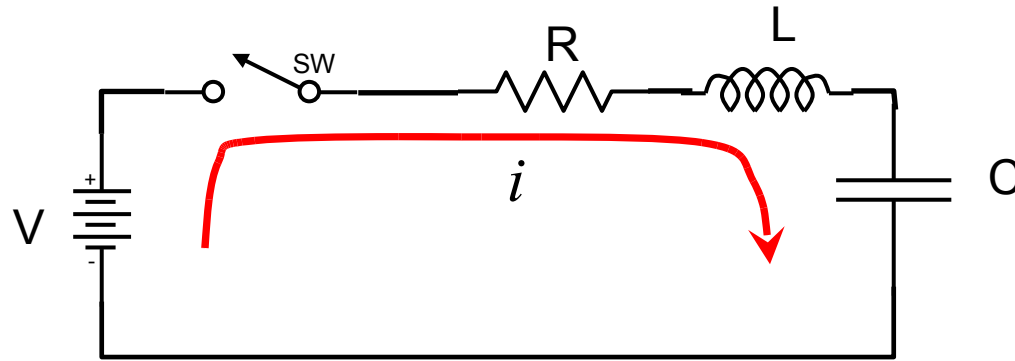


Transient Analysis: Series RLC Circuit




Current in an RLC circuit like shown is governed by the equation


$$\Rightarrow V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

We will analyse the situations with and without The source (V). The stored energy in C or L will force the current

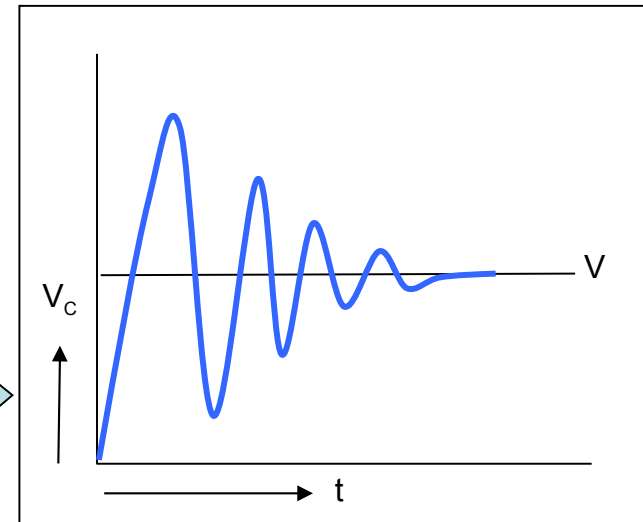
Once the switch (SW) is closed, after some oscillatory period, current And voltage will settle. In steady state, Capacitor voltage (V_c) will approach V \Rightarrow



LT SPICE Simulation: Adding components

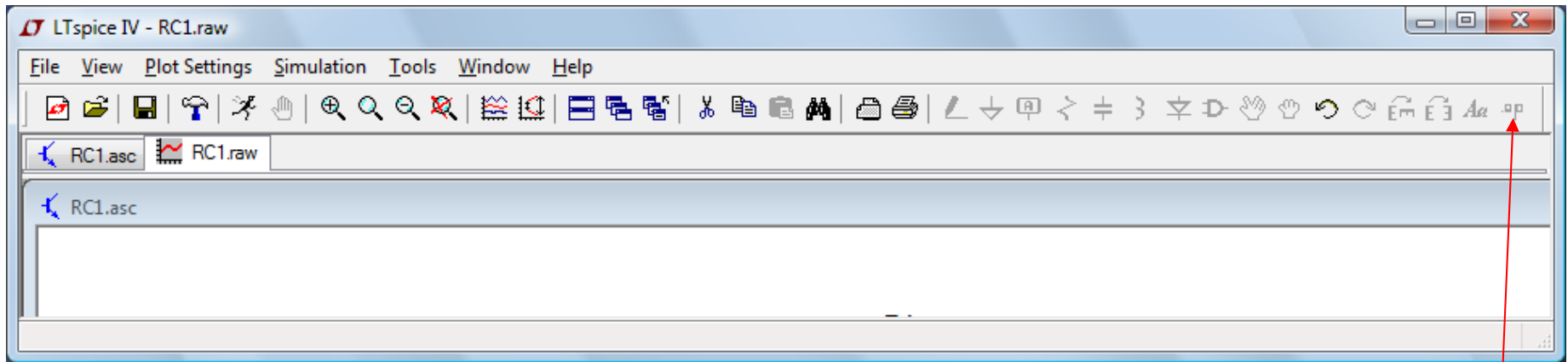

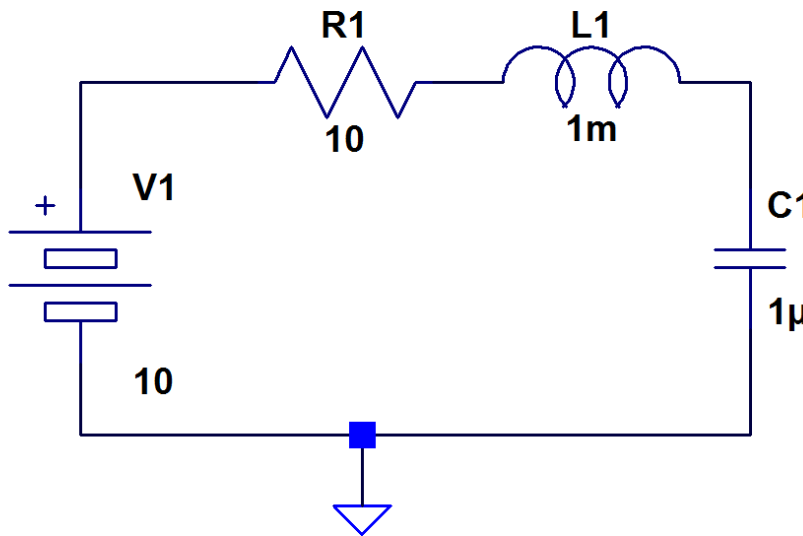After adding the component and components values , add the **SPICE DIRECTIVE**




`.IC I(L1)=0`

`.IC V(N003)=0`


`.tran 1ms`

Considering there is no stored energy in the inductor (L) or Capacitor, C


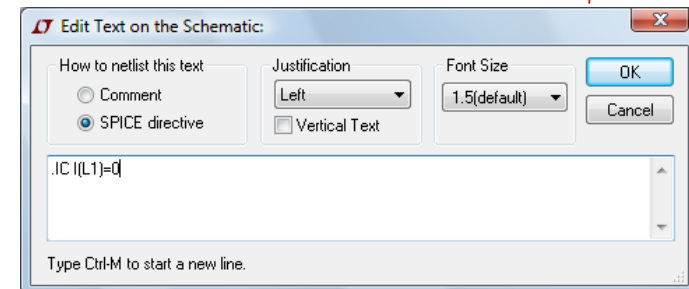
At time, $t=0$, $I = 0$
At time $t = 0$, $V_C = 0$



Run: Simulation

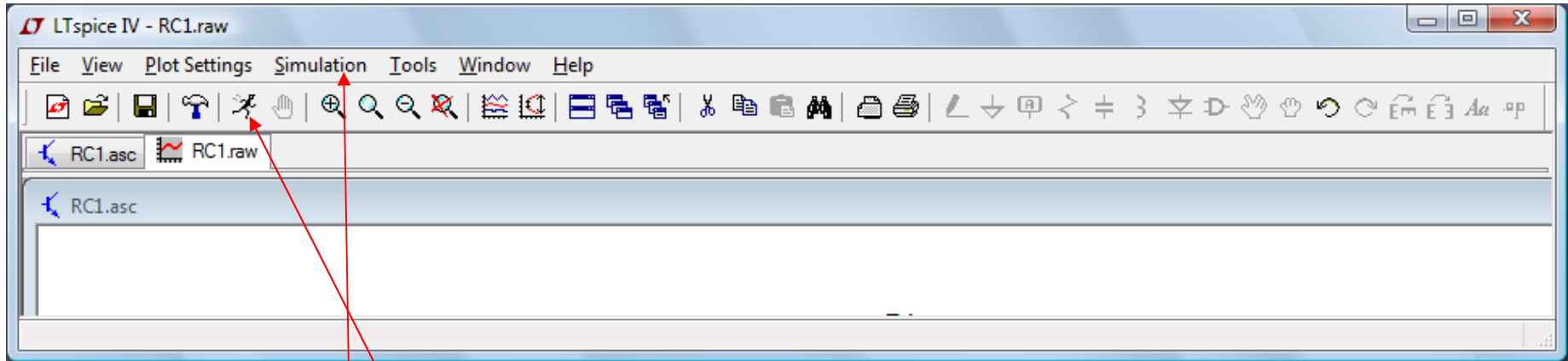


1. Simulation> Edit Simulation
2. RUN

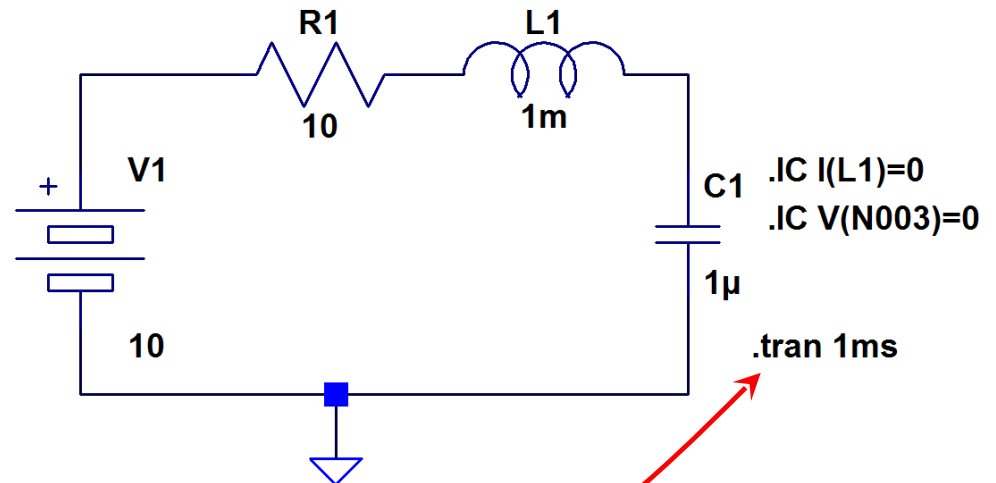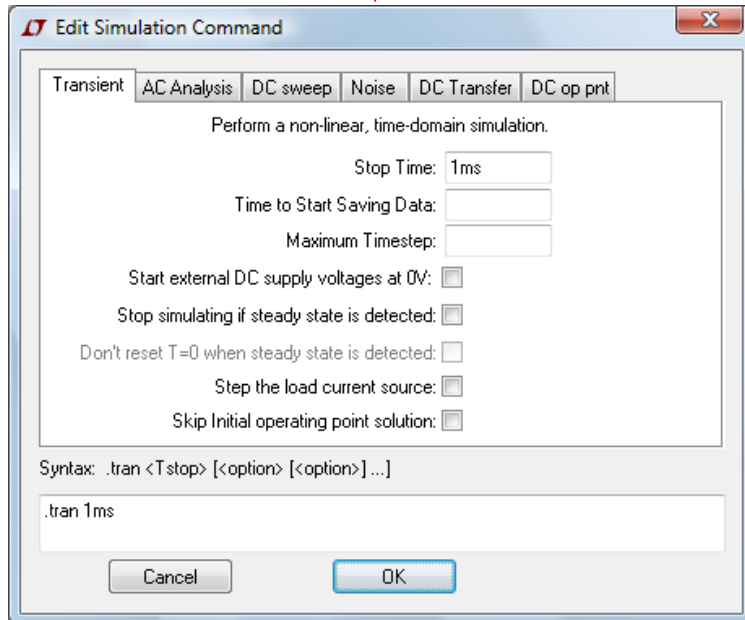


Run: Simulation

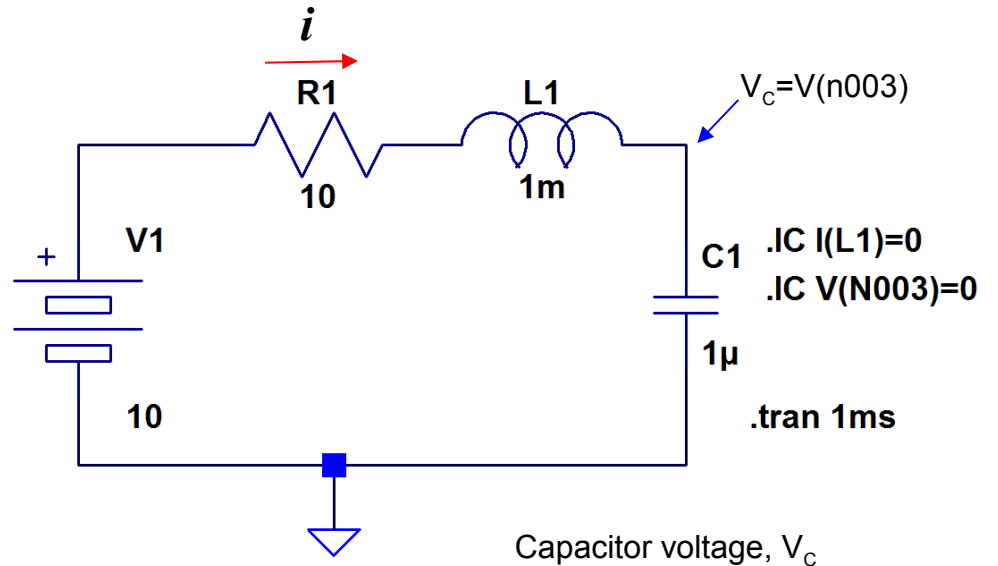
Running the simulation and placing the voltage probe at Node, n003 and clicking we find capacitor voltage and clicking the current probe either on R or L, we find current i




Current i

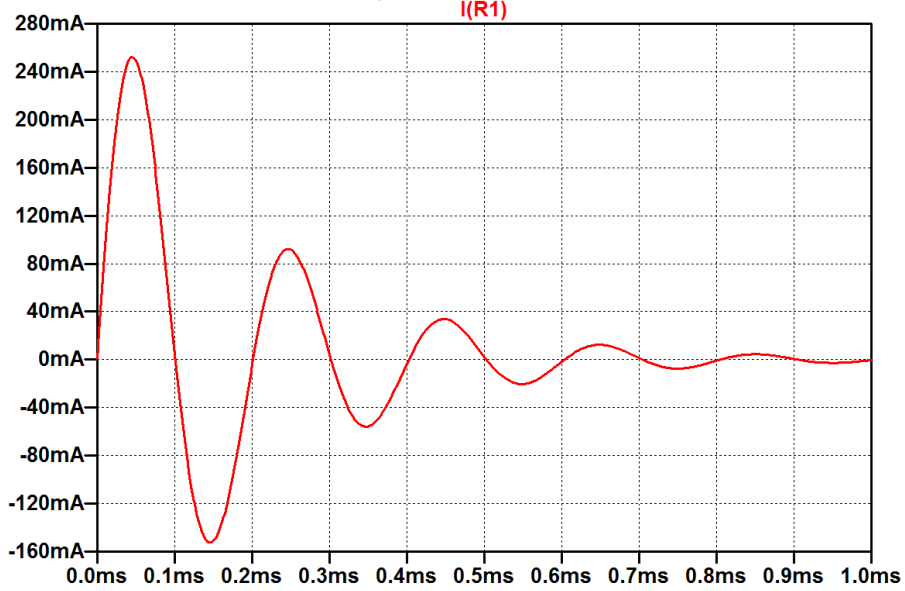

Capacitor voltage, V_C

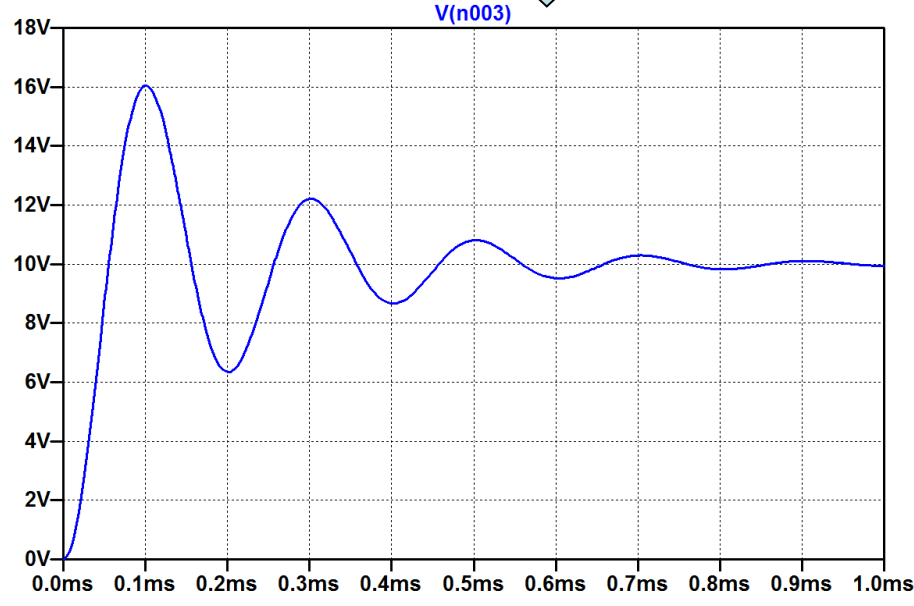

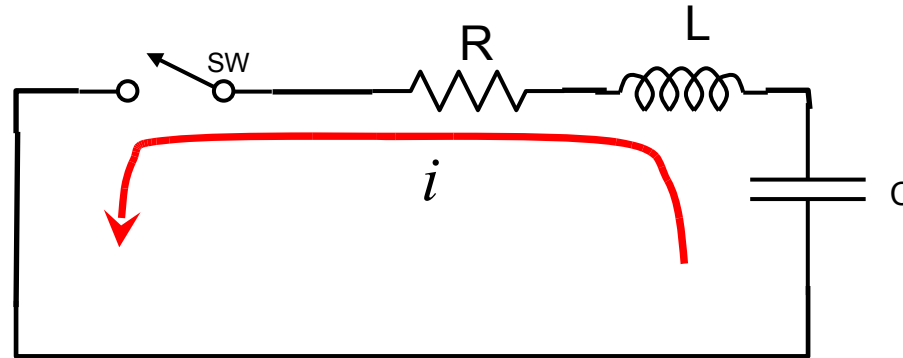
Stored Energy in Capacitor (C): No Power Source



When the capacitor is charged and connected as shown, energy will be exchanged back and forth in-between the inductor and capacitor. However the resistor will start dissipating the energy. The resulting current is governed by the equation

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$
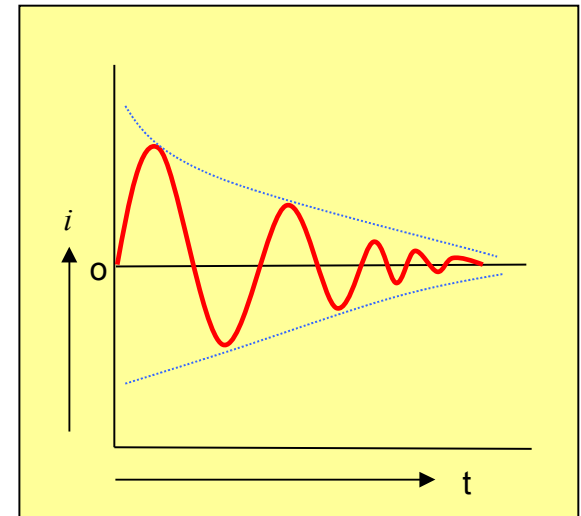
$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$



Simulation: Stored Capacitor in the Capacitor (C): No Power Source

The image shows the LTspice IV interface with a circuit diagram and three dialog boxes. The circuit consists of a resistor R1 (10 ohms), an inductor L1 (1mH), and a capacitor C1 (1μF) connected in series. The simulation command is `.tran 1ms`, and the initial conditions are `.IC I(L1)=0` and `.IC V(N002)=10`. The `.tran 1ms` command is circled in red. The `.IC V(N002)=10` command is also circled in red. The `.IC I(L1)=0` command is circled in red. The `.IC V(N002)=10` command is circled in red. The `.tran 1ms` command is circled in red.

Edit Simulation Command Dialog:

- Transient tab selected
- Stop Time: 1ms (circled in red)
- Time to Start Saving Data: [empty]
- Maximum Timestep: [empty]
- Start external DC supply voltages at 0V:
- Stop simulating if steady state is detected:
- Don't reset T=0 when steady state is detected:
- Step the load current source:
- Skip initial operating point solution:
- Syntax: `.tran <Tstop> [options] [options] ...`
- Input: `.tran 1ms`

Edit Text on the Schematic Dialog:


- How to re-list this text: SPICE directive
- Justification: Left
- Font Size: 1.5(default)
- Input: `.IC V(N002)=10`

Simulation Command:

- `.IC I(L1)=0`
- `.IC V(N002)=10`
- `.tran 1ms` (circled in red)

Put initial conditions using spice directive. `.IC V(N002)=10` means initial capacitor voltage is 10 V

Run Simulation

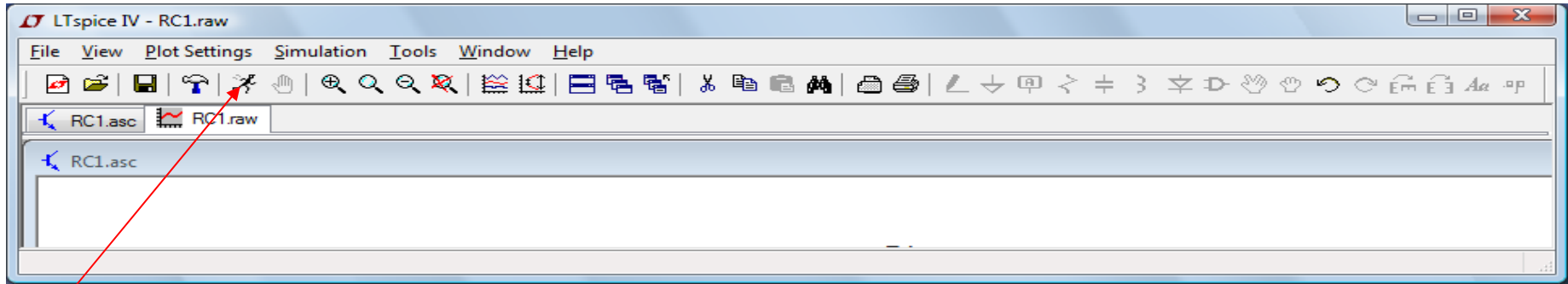


RUN



Running the simulation and placing the current Probe on either the resistor or the inductor, we find the oscillatory current as shown




Current

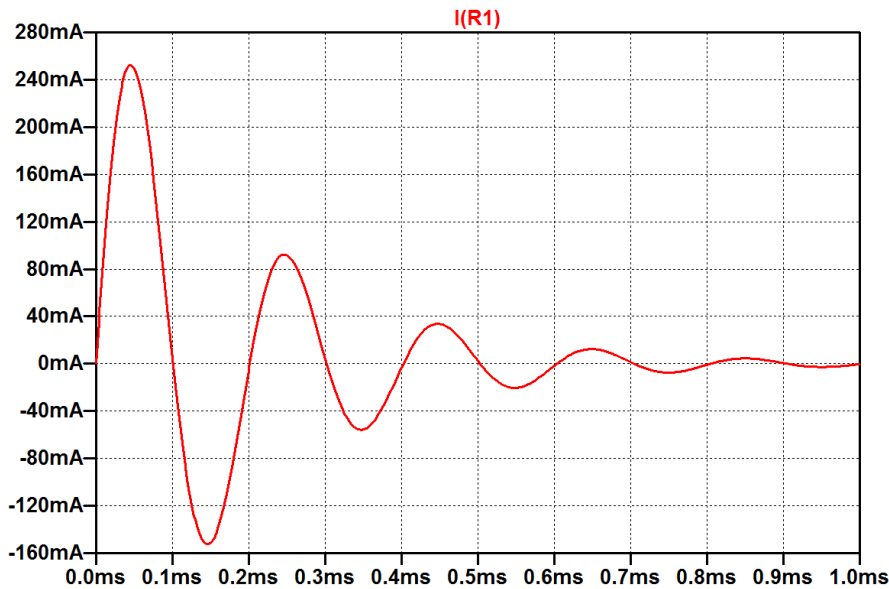


Placing the voltage probe at node:N002 and Clicking we find the capacitor voltage waveform



Capacitor voltage

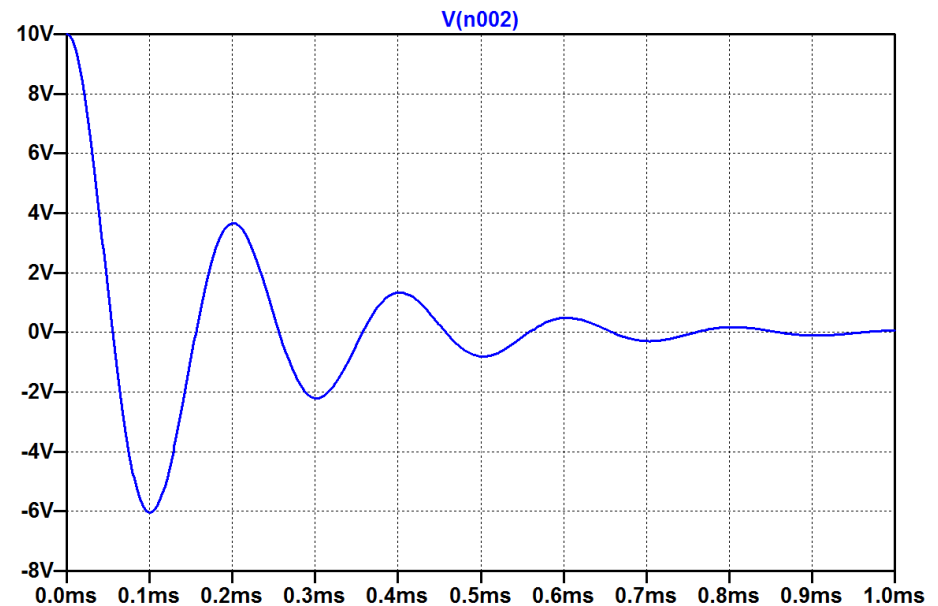

LTSpice to find Power and energy

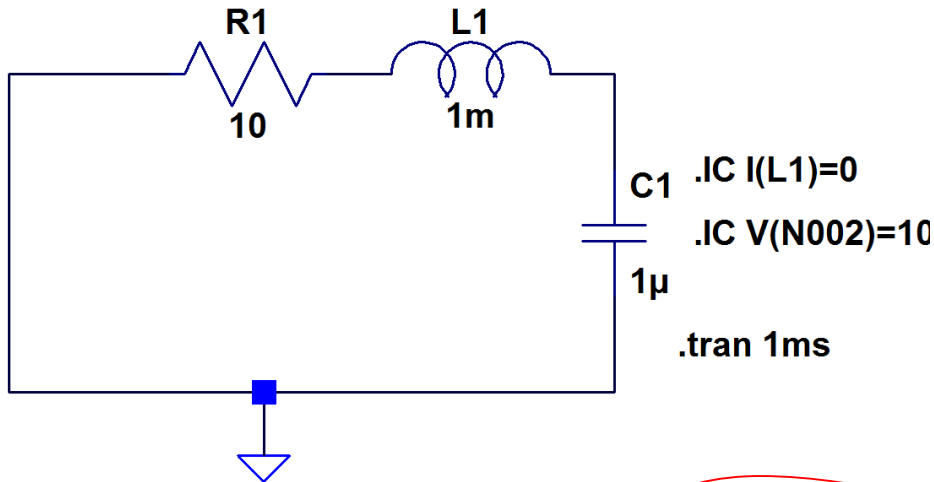

Press down **ALT** and put the cursor on R1 (You will see a thermometer icon) and click





You will get the power data as shown



Press down **CTRL** and place the cursor on $V(N001)*R1$ as shown and click

You will get the window like this

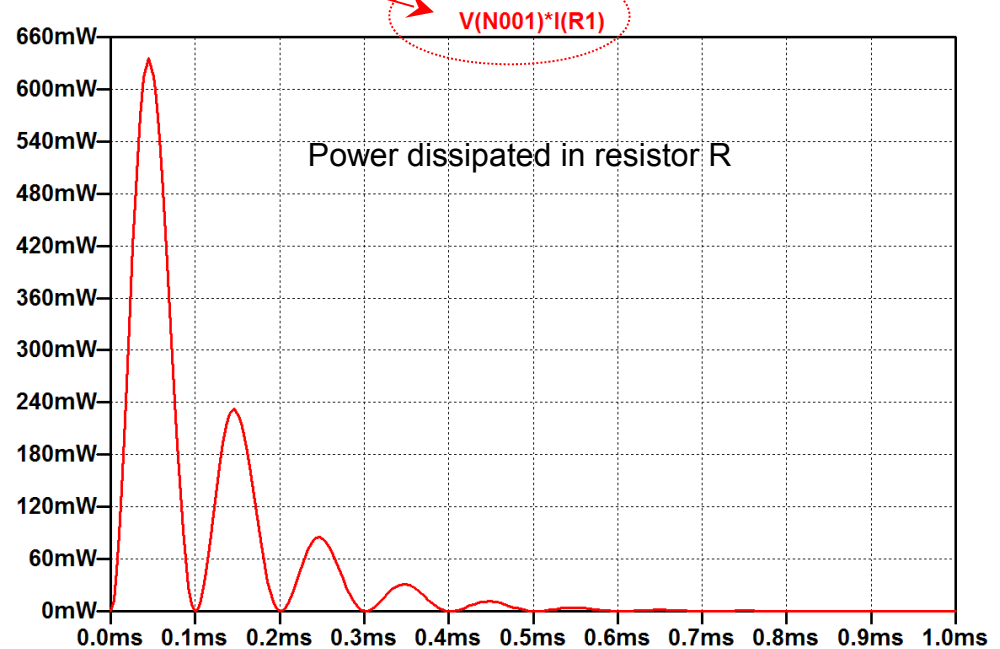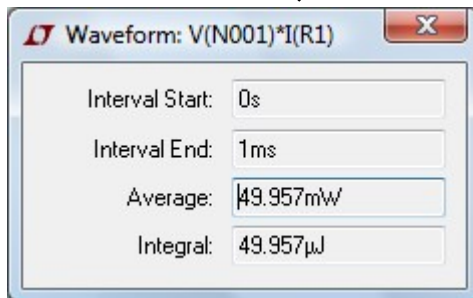


Stored Energy in Inductor (L): No Power Source

When the switch in position 1, maximum current V/R_L reaches in steady state. Now the switch is placed in position 2, the stored energy in the inductor will cause the current to oscillate in the LRC circuit.



In practice: Whenever the switch is about to release from position 1, there will be abrupt change in current, causes a high voltage to develop governed by the equation: $V_L = L di/dt$. The stored energy in the inductor ($1/2 LI^2$) will be lost at the switch junction (1) (high voltage > Ionization > arcing (heat)). However by electronic devices it is possible to release inductor-energy into an LRC circuit. I hope to discuss it later

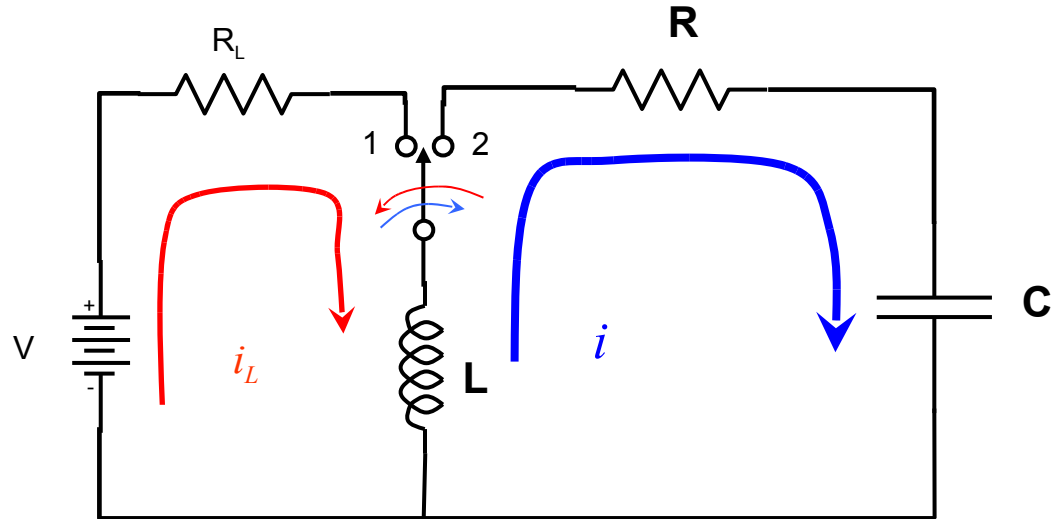


$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$


Nature of current can be expressed by the equation

However Let us consider an idealised situation that when the switch is in position 2 the energy ($1/2 LI^2$) is released in the LRC circuit

LT SPICE Simulation: Adding components

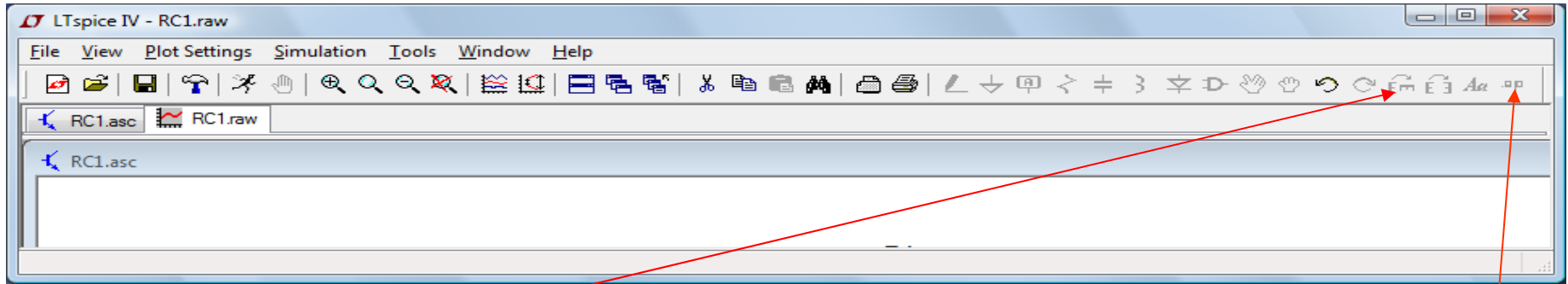

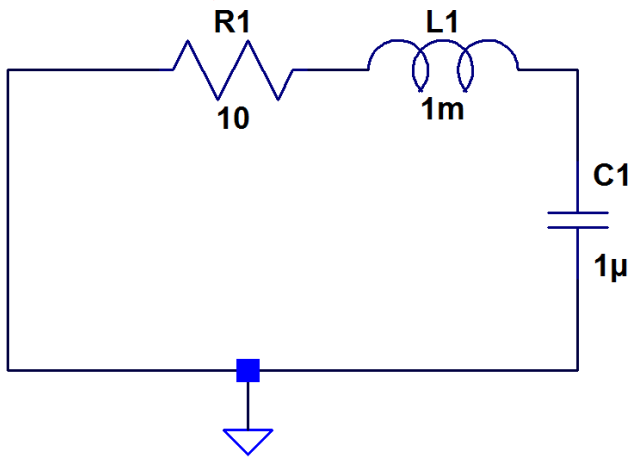
Rotate resistor R1 twice, which will give you the current in positive direction




```
.IC I(L1)=1  
.IC V(N002)=0  
  
.tran 1ms
```

Now initial inductor current is 1 Amp. and the capacitor voltage is 0 V

Set the spice directive

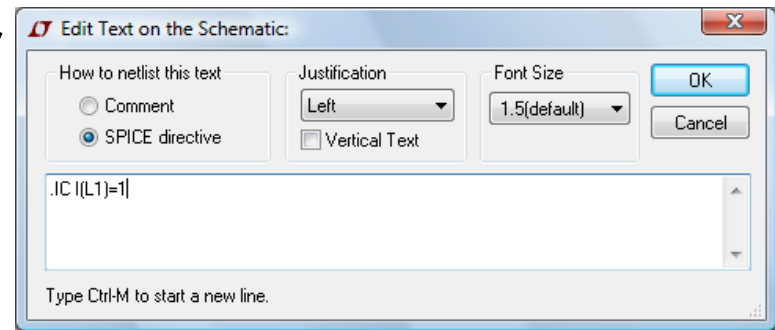

RUN: Simulation

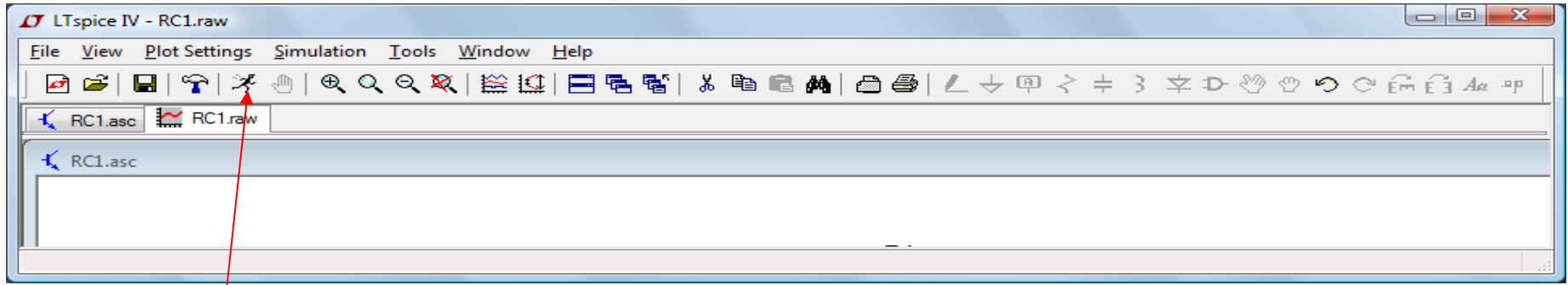

Run the simulation





We get current and capacitor voltage as shown:

Current




Capacitor voltage


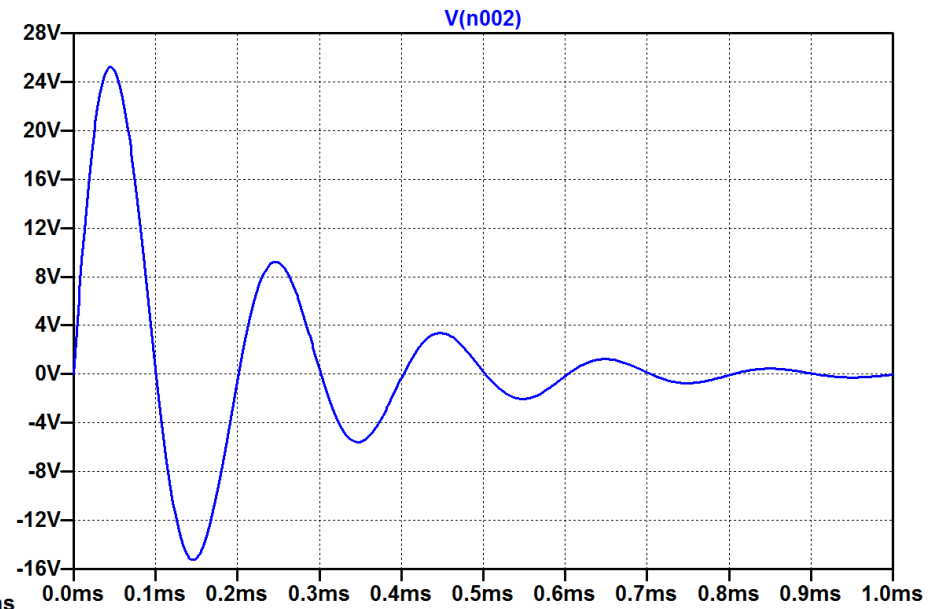
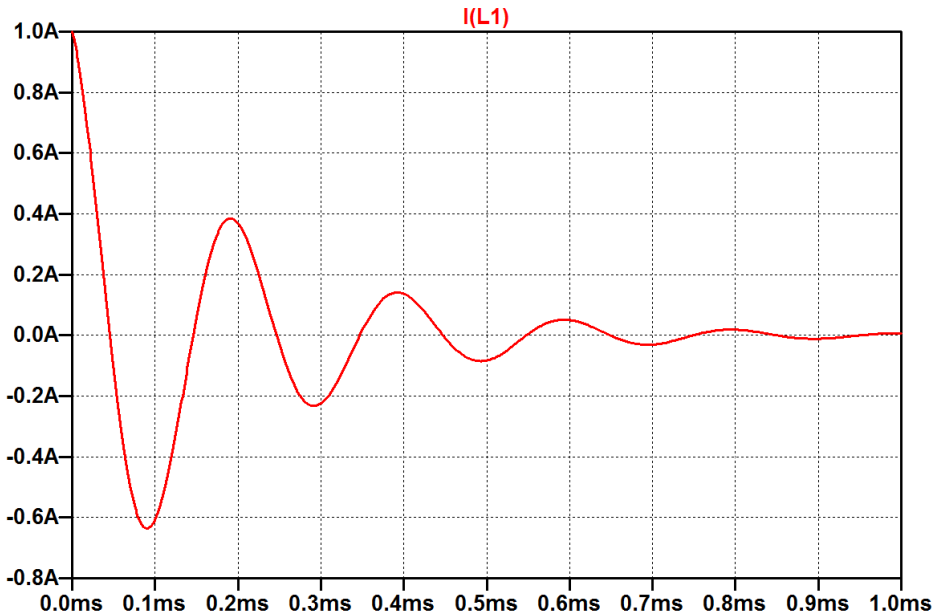


LTSpice to find Power and energy

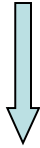Press down **ALT** and put the cursor on R1 (You will See a thermometer icon) and click




You will get the power data as shown

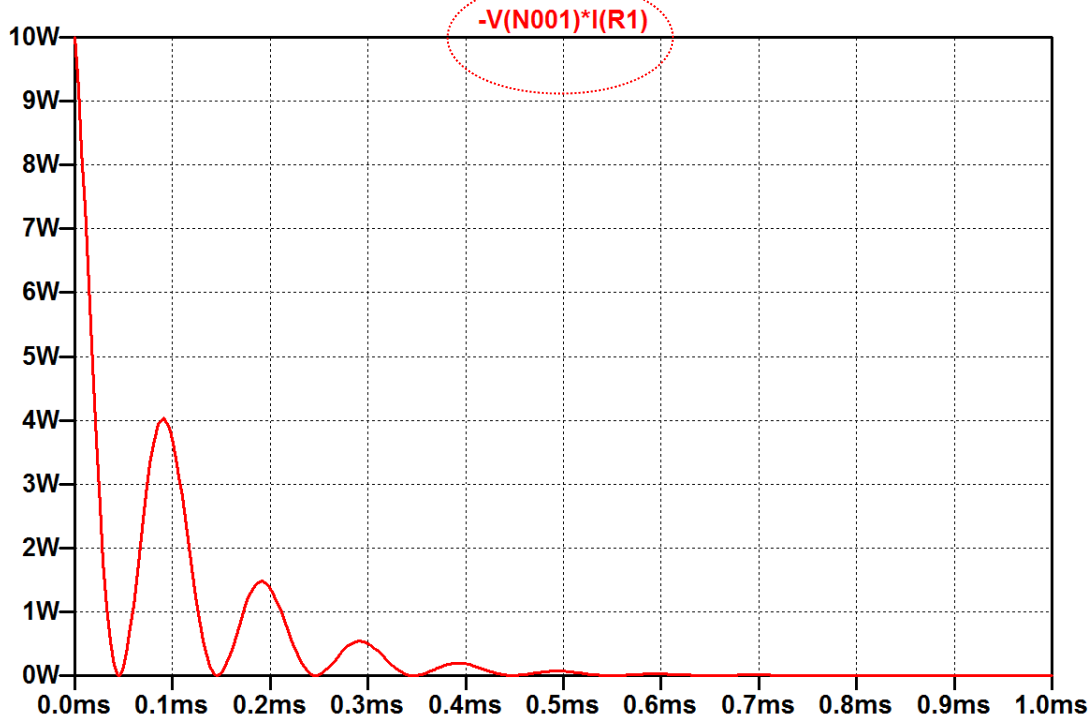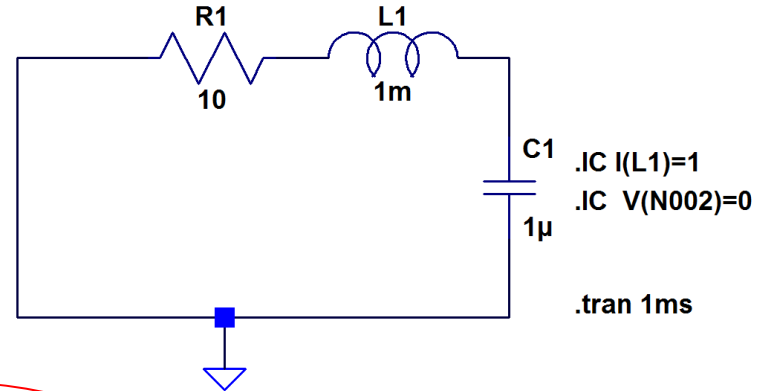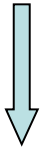

Press down **CTRL** and place the cursor on $V(N001)*R1$ as shown and click



You will get the window like this

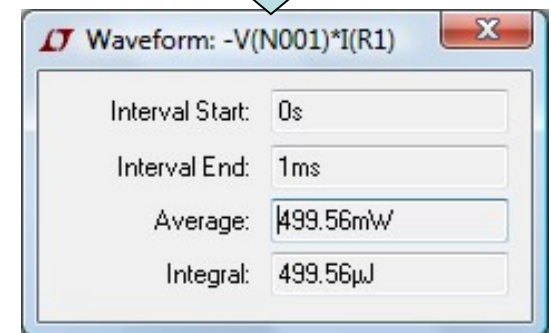

Under, over and Critically damped oscillation in LRC circuit

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0 \quad \boxed{1}$$

Let us consider: $i = A e^{st}$ $\boxed{2}$

Putting equation 2 in 1:

$$L S^2 A e^{St} + R S A e^{St} + \frac{i}{C} = 0$$

$$A e^{st} \left[L S^2 + R S + \frac{1}{C} \right] = 0$$




This is the characteristic equation
Which determines the circuit behaviour

Roots of this equation:

$$S_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$
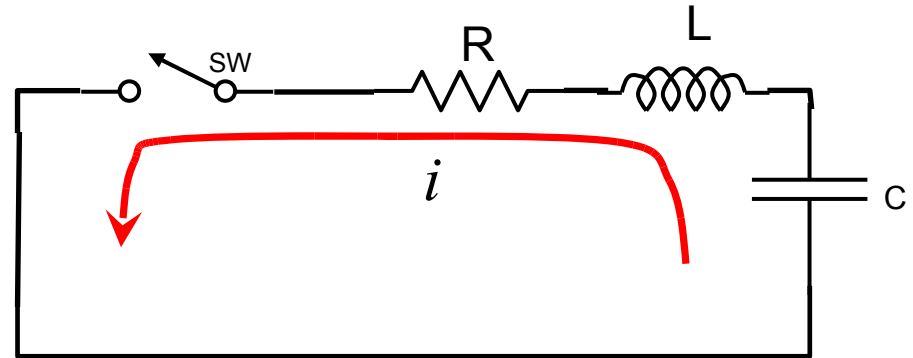
$$S_1 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC} \quad \leftarrow \text{Overdamped}$$

$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC} \quad \leftarrow \text{Underdamped}$$

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC} \quad \leftarrow \text{Critically damped}$$

Under, over and Critically damped oscillation in LRC circuit

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

The solutions of the differential equation for these three conditions:

Overdamped

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$




$$\alpha^2 > \omega_0^2$$

$$i(t) = Ae^{s_1 t} + Be^{s_2 t}$$

Where, $s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

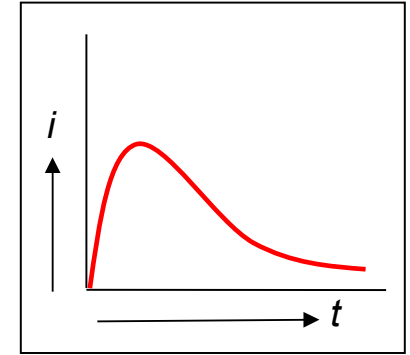Let us consider, $\alpha = \frac{R}{2L}$ And $\omega_0 = \frac{1}{\sqrt{LC}}$




Underdamped

$$\alpha^2 < \omega_0^2$$

$$i(t) = e^{-\alpha t} (A \cos \omega t + B \sin \omega t)$$

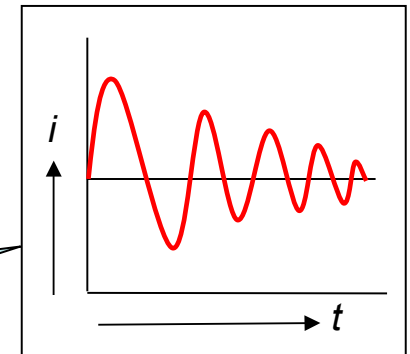
Where $\omega = \sqrt{\omega_0^2 - \alpha^2}$




Critically damped

$$\alpha^2 = \omega_0^2$$

$$i(t) = (A + Bt) e^{-\alpha t}$$

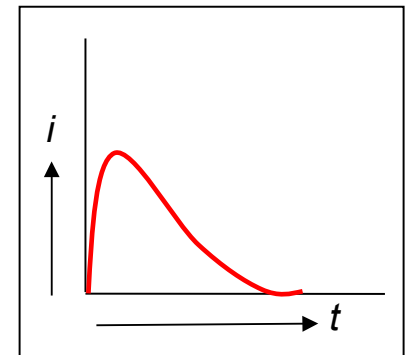

Simulation - Undamped: LTSpice

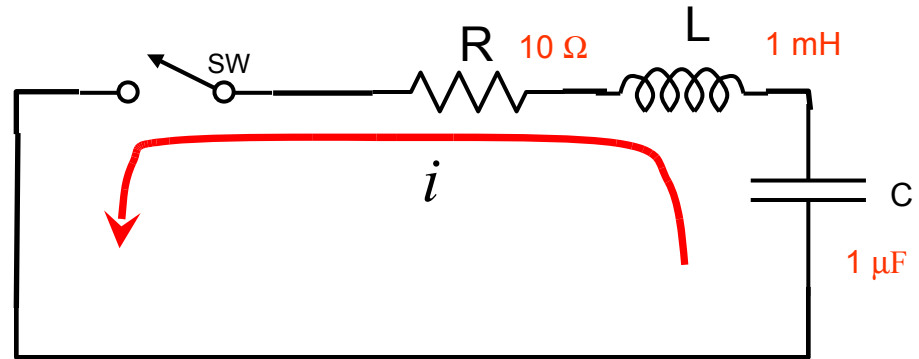

$$\left(\frac{R}{2L}\right)^2 = 25 \times 10^6$$

$$\frac{1}{LC} = 1 \times 10^9$$

$$\text{As, } \left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$


It is a case of underdamped oscillation as we found before

$$i(t) = e^{-\alpha t} (A \cos \omega t + B \sin \omega t)$$

$$\omega = \sqrt{\omega_o^2 - \alpha^2}$$

$$= 31224.99 \text{ Rad/sec}$$
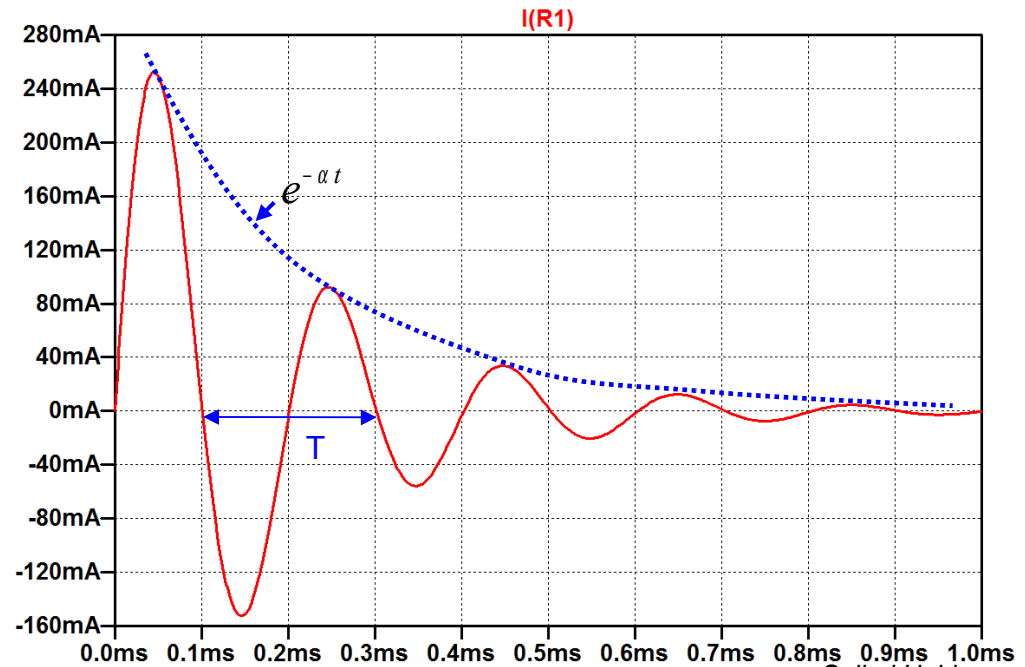
$$\text{Time period, } T = \frac{2\pi}{\omega} = 201.2 \mu\text{s}$$



Simulation - Overdamped: LTSpice

Let us consider, $R=200\ \Omega$



$$\left(\frac{R}{2L}\right)^2 = 1 \times 10^{10}$$

$$\frac{1}{LC} = 1 \times 10^9$$

$$\therefore \left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

$$i(t) = Ae^{s_1 t} + Be^{s_2 t}$$

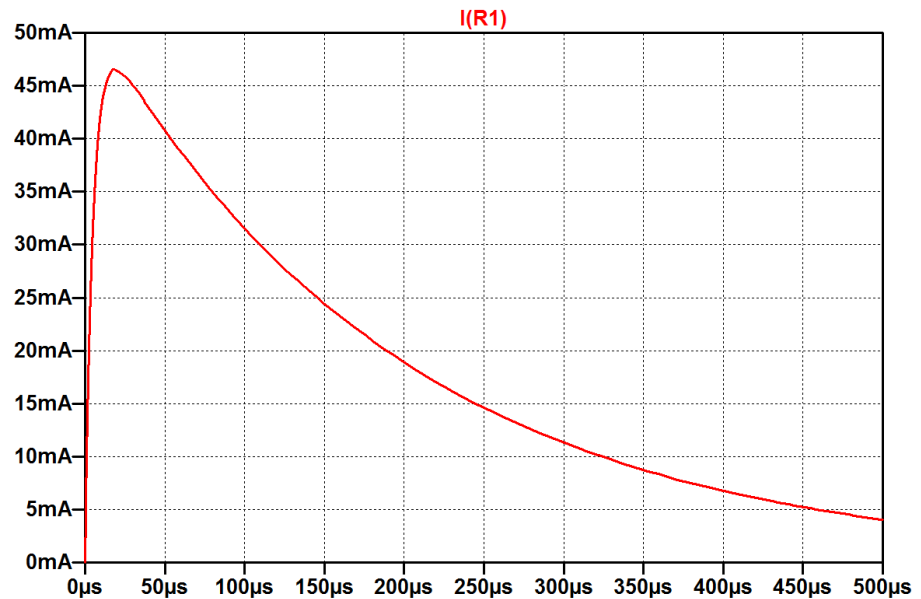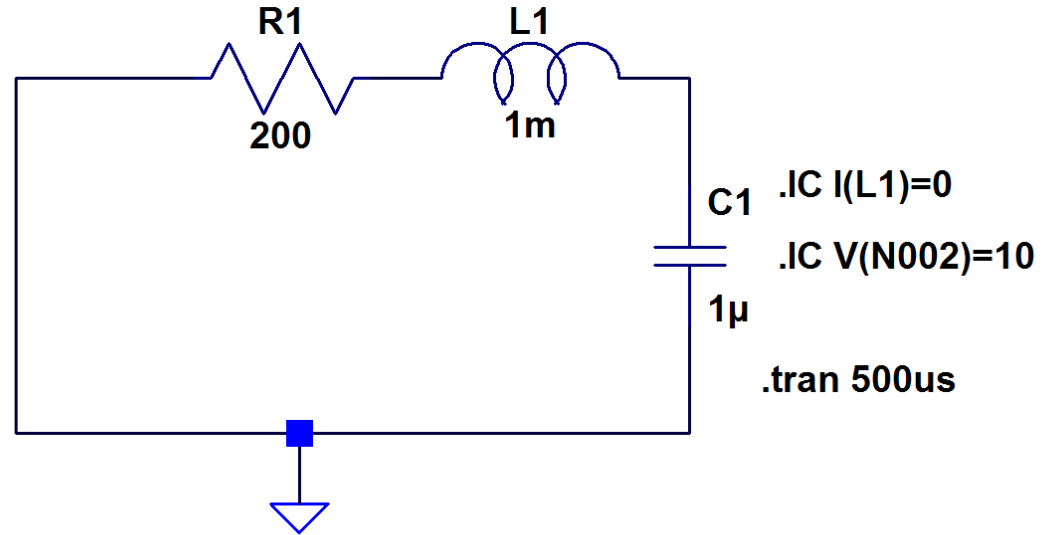Running LTSpice simulation the same way as
Before we find the overdamped behaviour as shown



Simulation - Critically Damped: LTSpice

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

$$\alpha^2 = \omega_0^2 \quad \text{Or} \quad \left(\frac{R}{2L} \right)^2 = \frac{1}{LC}$$

In our case with, $L = 1\text{mH}$, $C = 1\mu\text{F}$:

$$R = 63.245 \Omega$$


$$i(t) = (A + Bt) e^{-\alpha t}$$

To find the time at which the current reaches the peak, we should differentiate $i(t)$ and equate to 0:

$$\frac{di(t)}{dt} = 0$$

$$t_c = \frac{1}{\alpha} = \frac{2L}{R} \quad \text{Putting } R = 63.245 \Omega$$

$$t_c = 31.62 \mu\text{s}$$

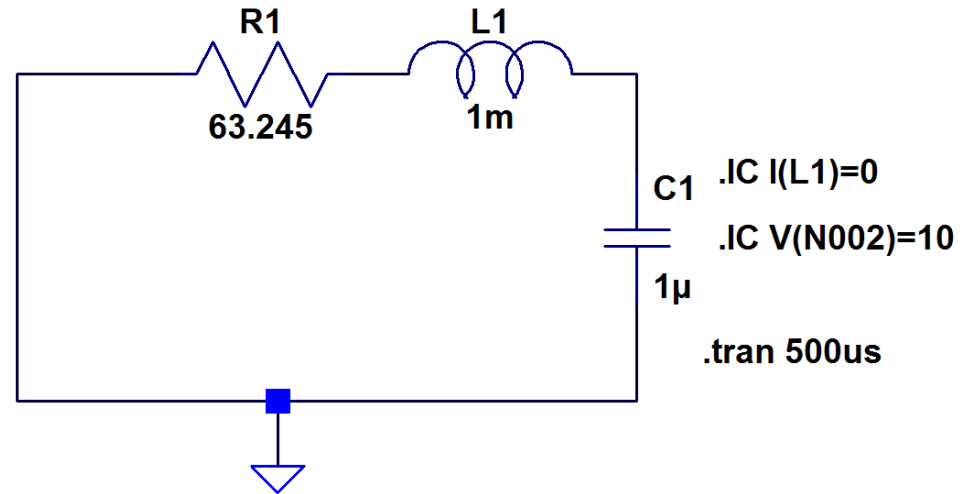


Simulation - Critically Damped: LTSpice

Running the simulation gives us the current response, $i(t)$ as shown



I(R1)

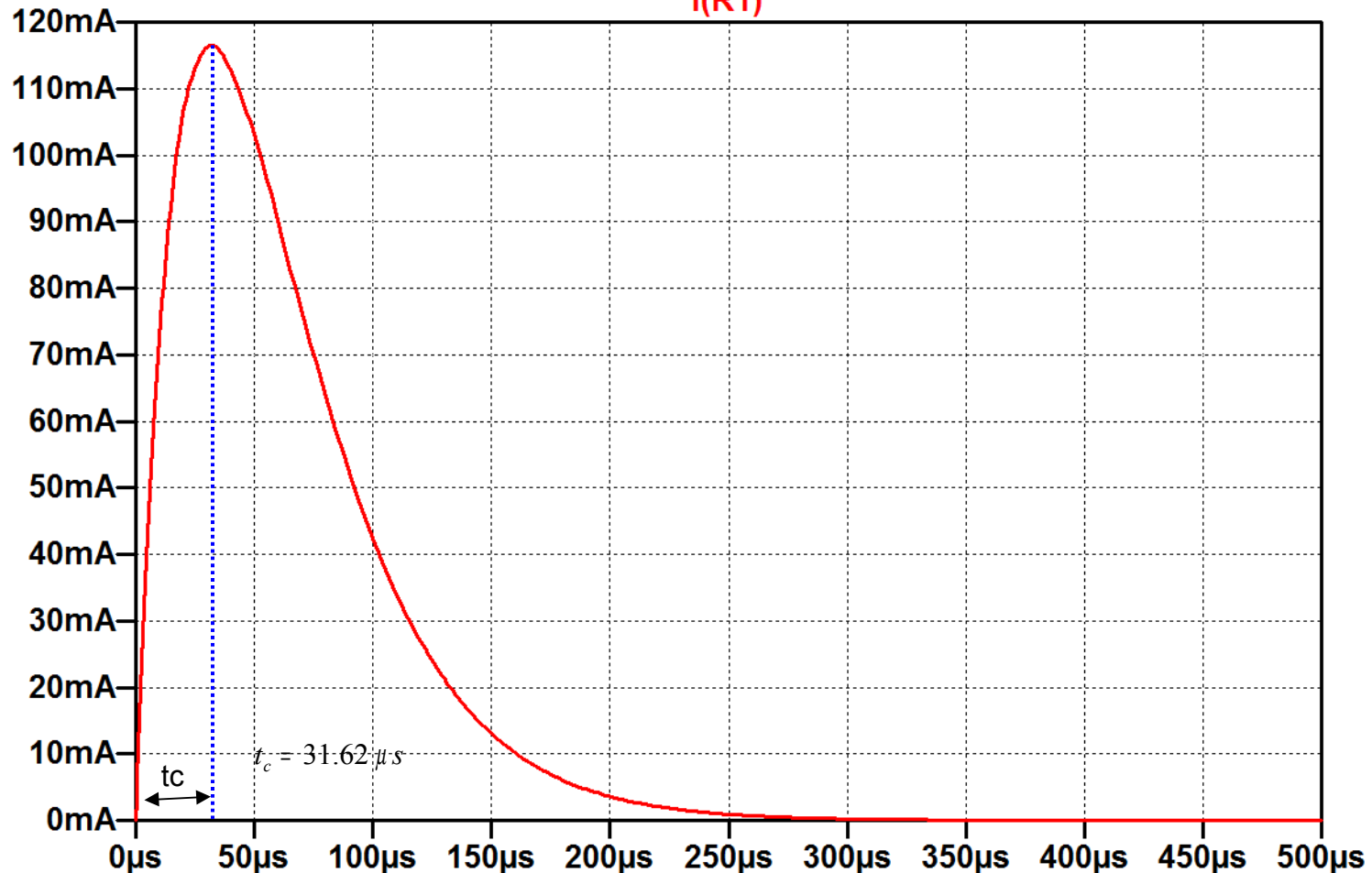

The importance of critically damped circuit is, current quickly reaches 0 without oscillating