
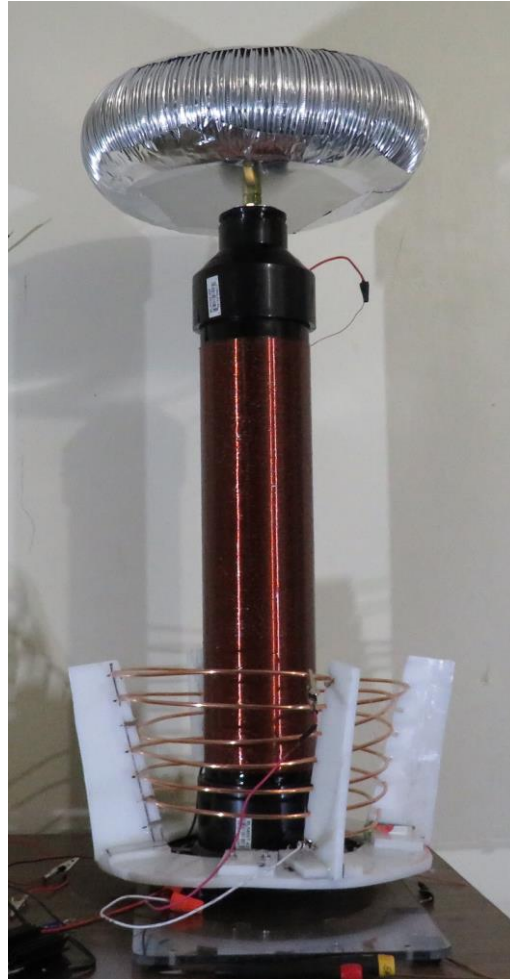


Basics of Tesla Coil

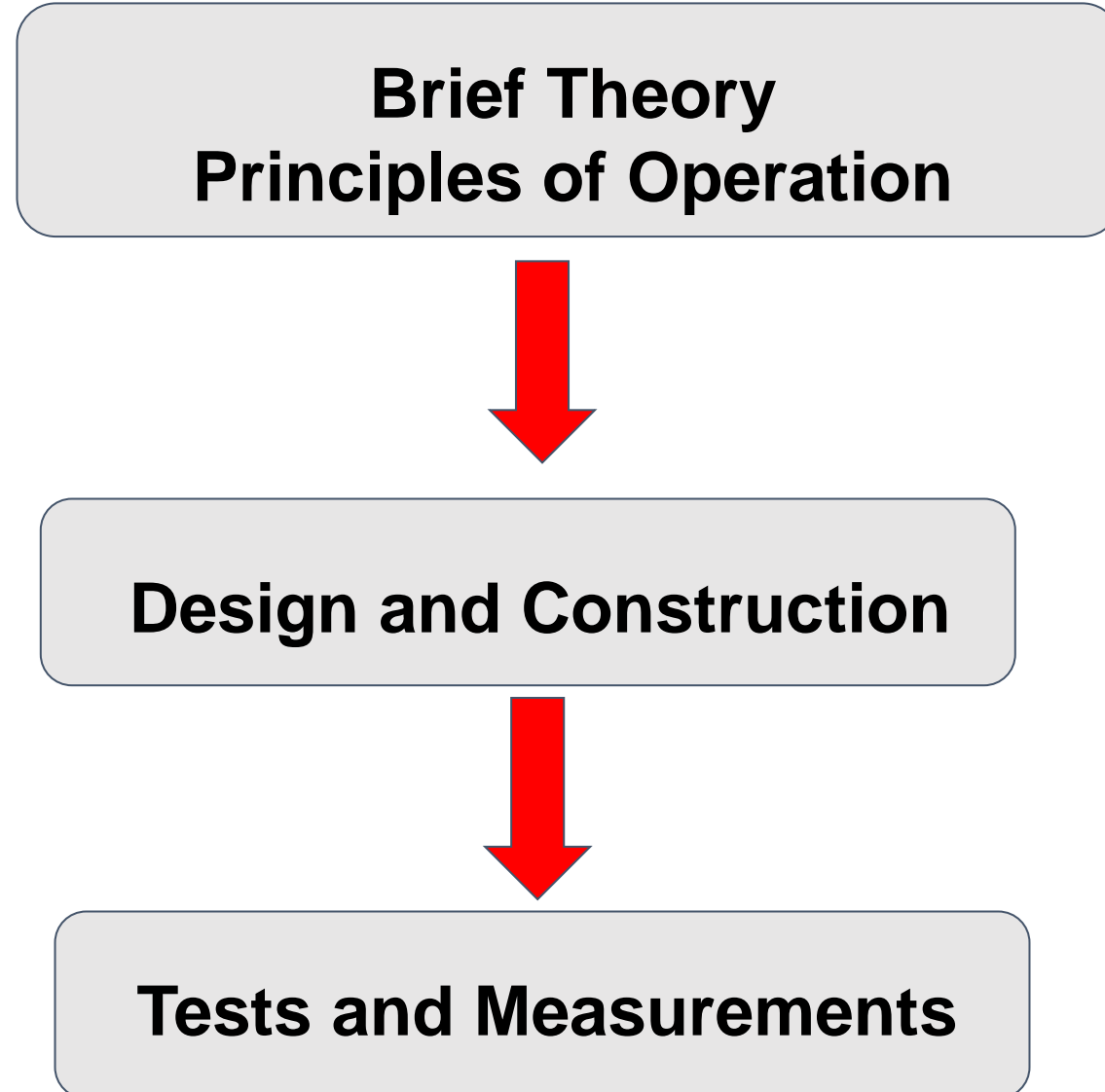

Make Your Own Tesla Coil


Sequence



Theory: What you need

1. Knowledge of Basic LRC Circuit : Transient and AC Response
2. Circuit Analysis Software:

LTSpice

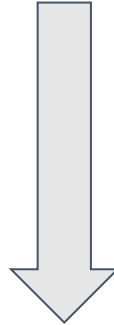


Download and use it for free

<https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

Tesla Coil: Not an Ordinary Transformer


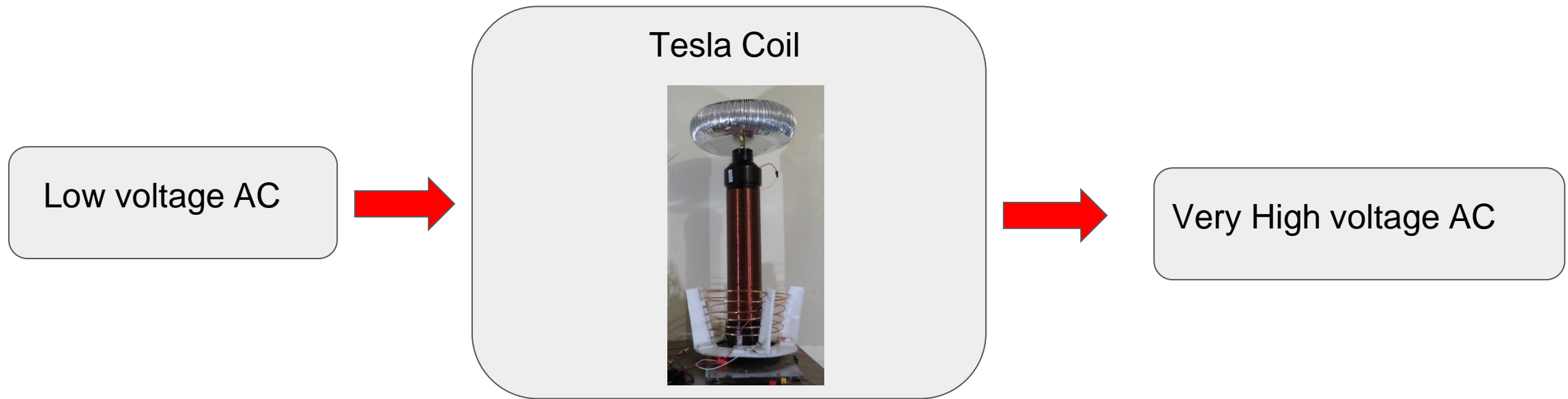
Though it looks like a transformer, however not an ordinary one. Energy is transferred from the primary to the secondary by carefully adjusting the ***coupling*** and the secondary is tuned at ***resonance*** to achieve maximum voltage



Uses two effects: Resonance and Coupling

A Simple LRC Series Circuit and Resonance

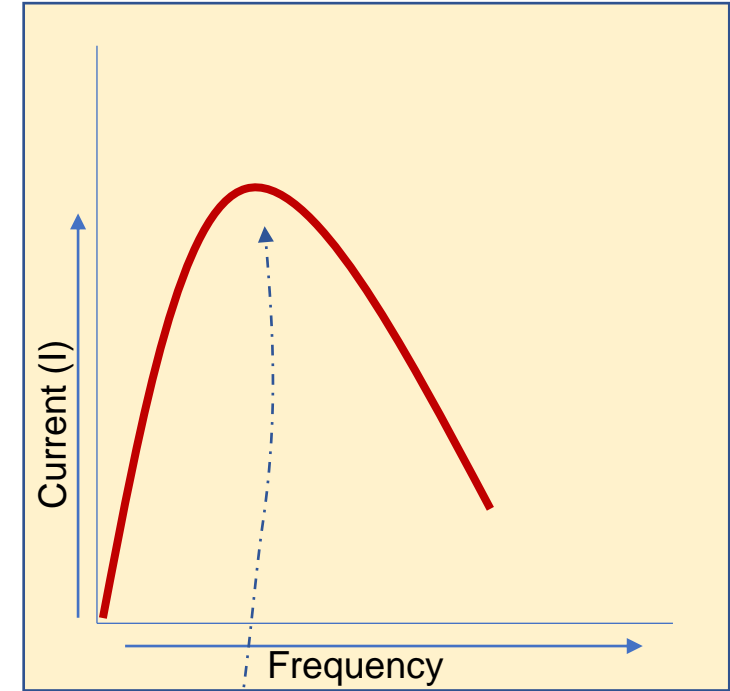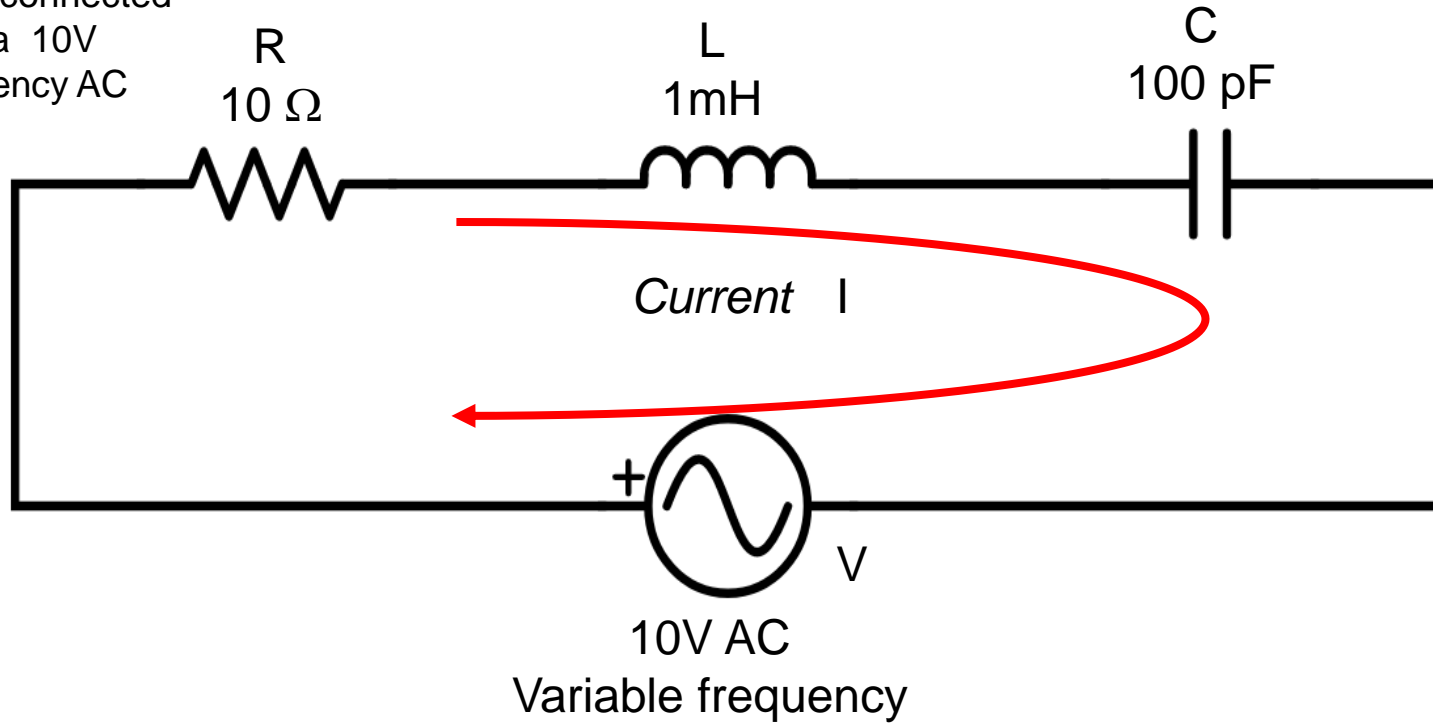An inductor, a capacitor and a resistor connected in series with a 10V variable frequency AC source



Impedance (z) of series LRC:

$$z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$I = \frac{V}{Z}$$

At resonance:

$$\omega L - \frac{1}{\omega C} = 0$$

$$I = \frac{V}{R}$$


Analysing The LRC Circuit with LTSpice

At resonance


$$z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\omega L = 1/\omega C$$


$$I = V/R$$

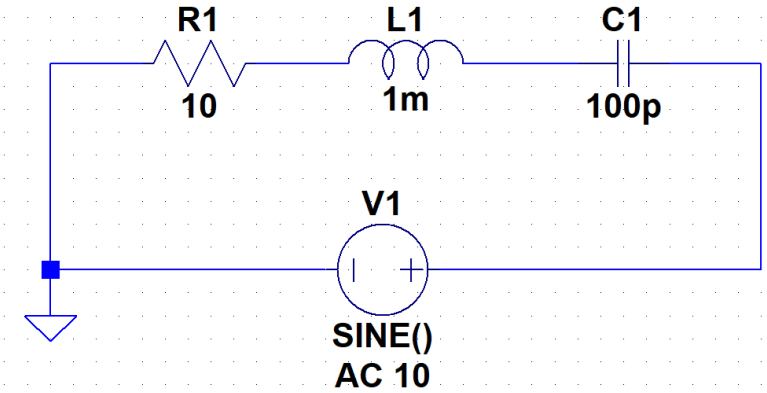

```
.ac lin 100000 400000 600000
```

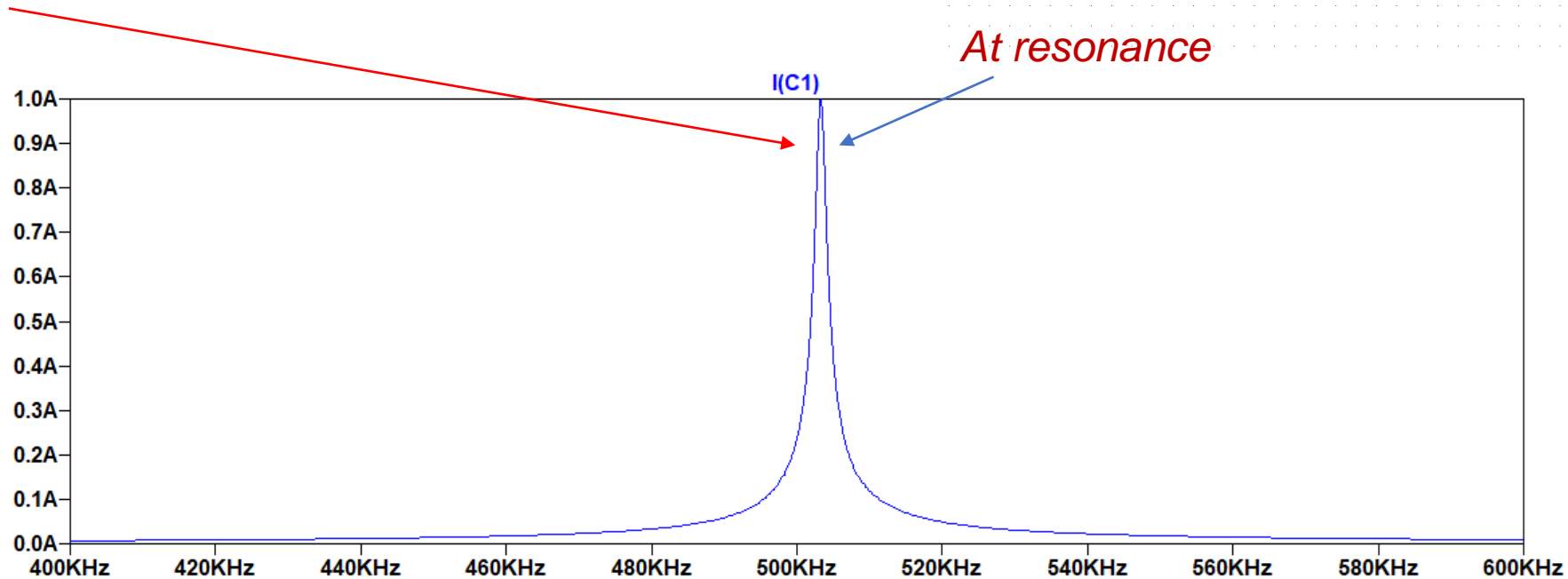


Voltage Across Capacitor

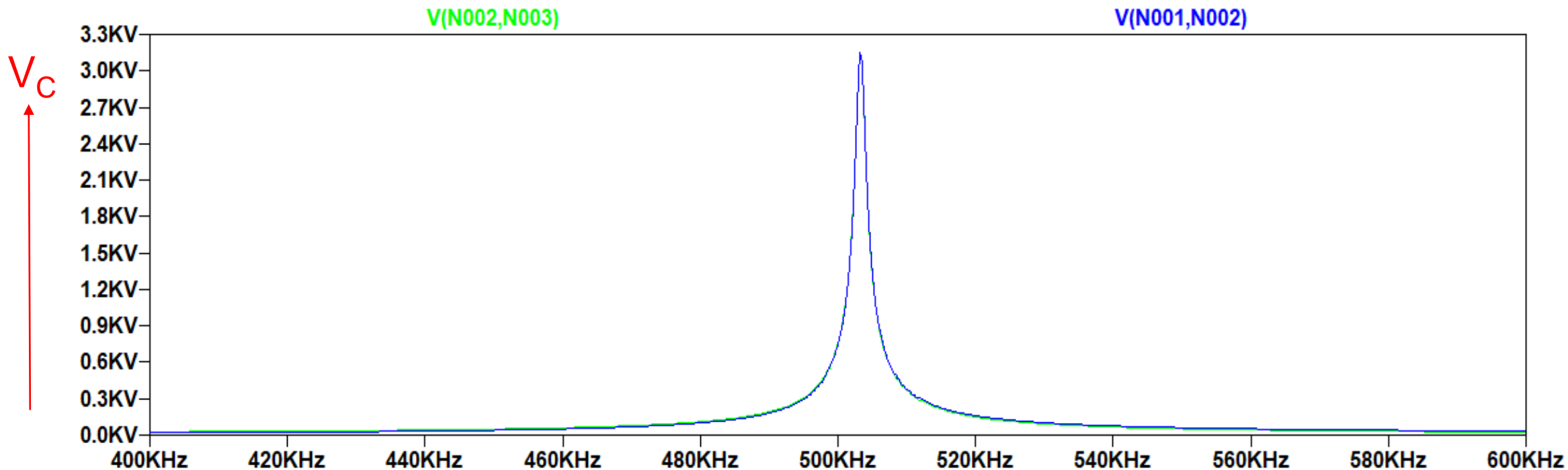

Lower the value of C Higher the voltage V_C

$$V_C = I/\omega C$$

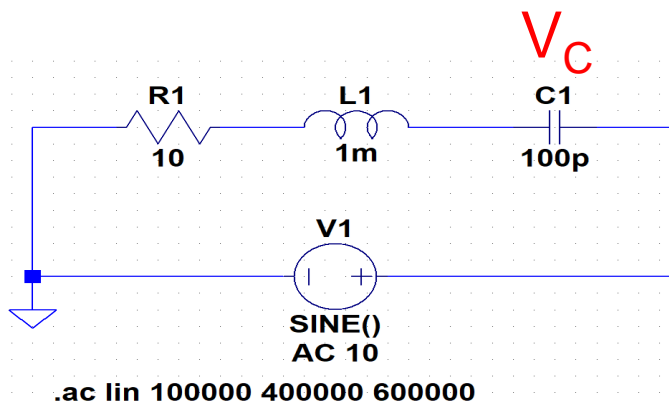



Voltage Gain

Simulation shows, voltage at the point



$$V_C = 3\text{kV}$$

Supply voltage: 10 V

$$\text{Gain: } 3000/10 = 300$$

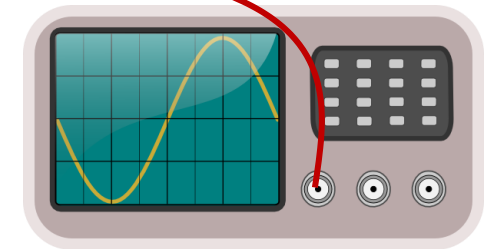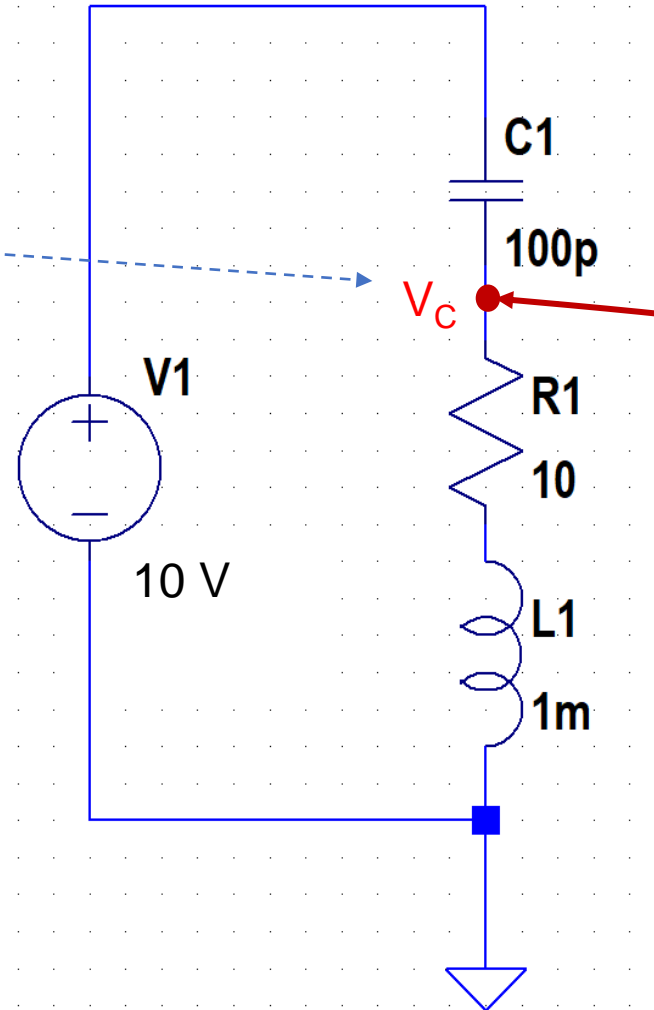

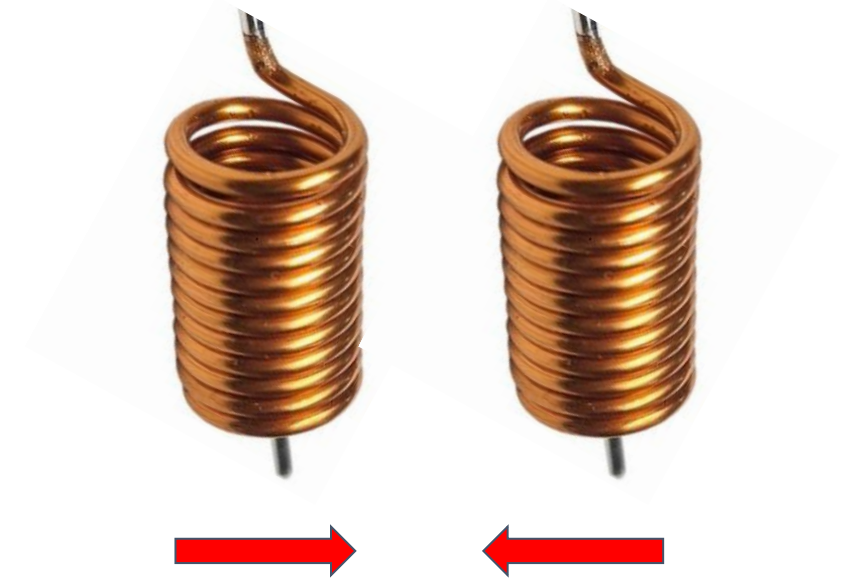
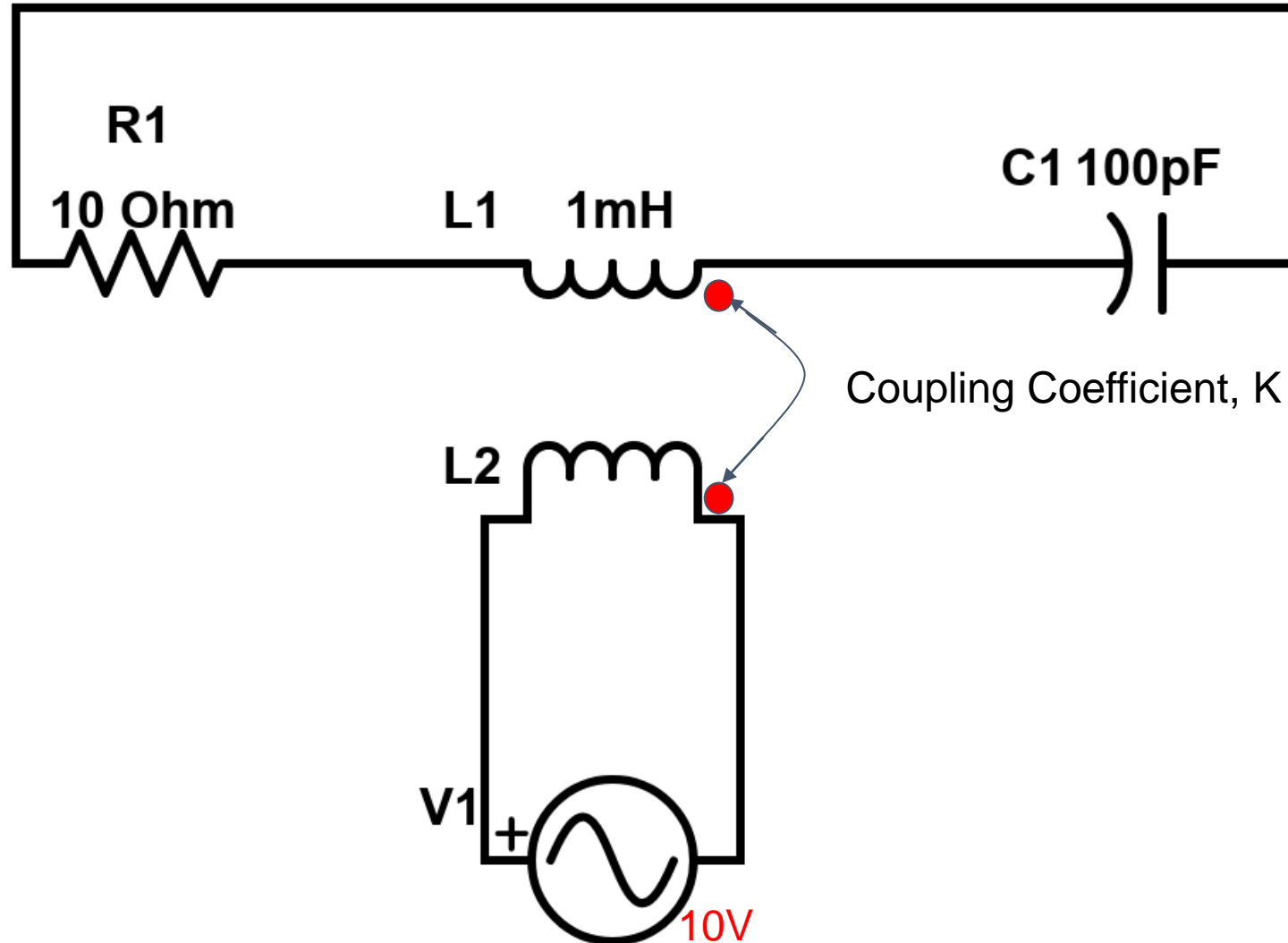
AC Source Replaced by Transformer Coupling




Closer: Tighter coupling, K
Maximum $K = 1$

Simulation of a Coupled Circuit

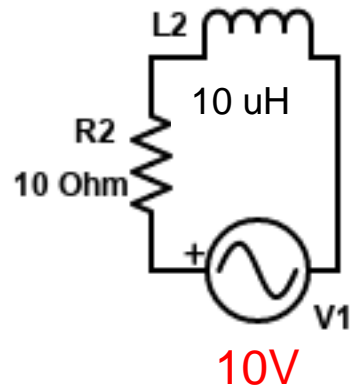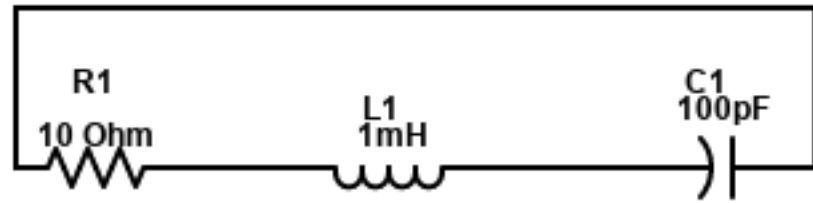Considering Primary-coil (L2) Inductance = $10\ \mu\text{H}$



LTSpice

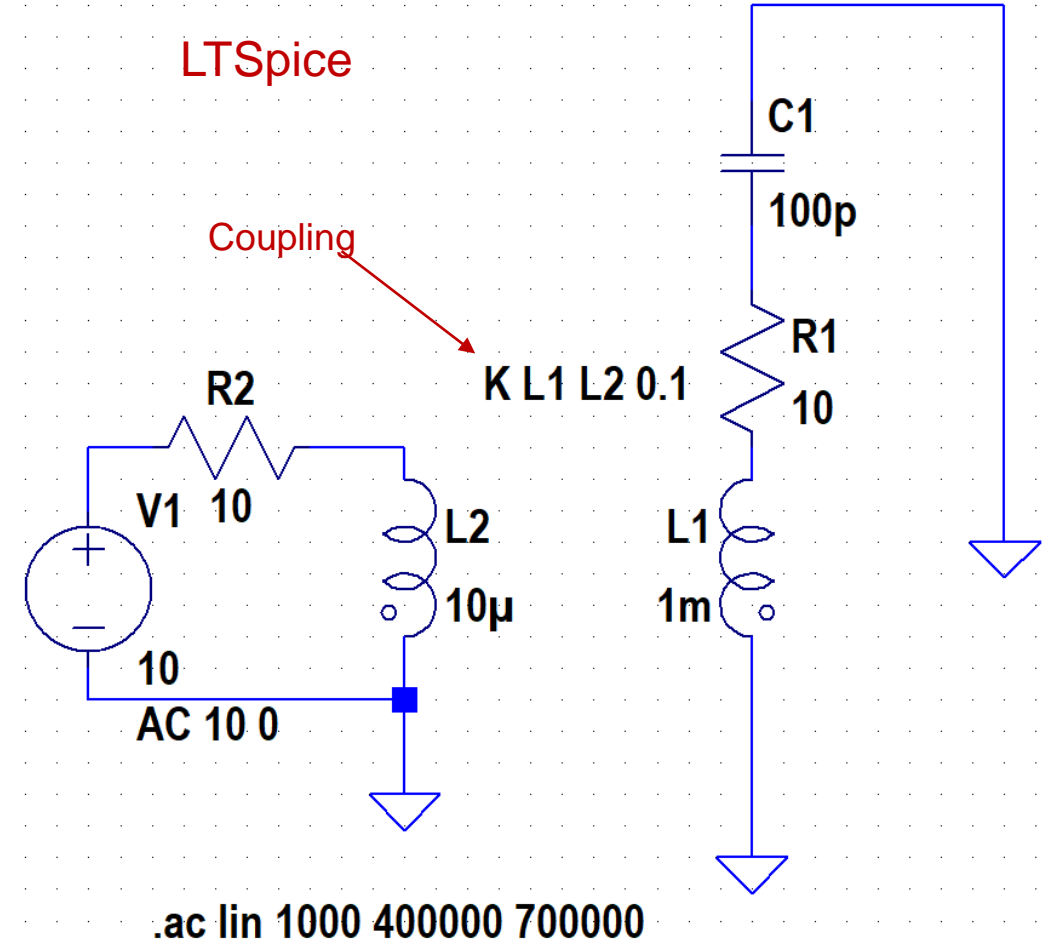

$10\ \Omega$ is added to limit the current to 1 A

Instead of Source, Energy Supplied by Transformer Coupling

Our goal is to get maximum voltage at the secondary




**Coupling, $K \sim 0.1$
Gives best result**




For tighter coupling ($K=1$): Energy is transferred to Secondary and part of that comes back

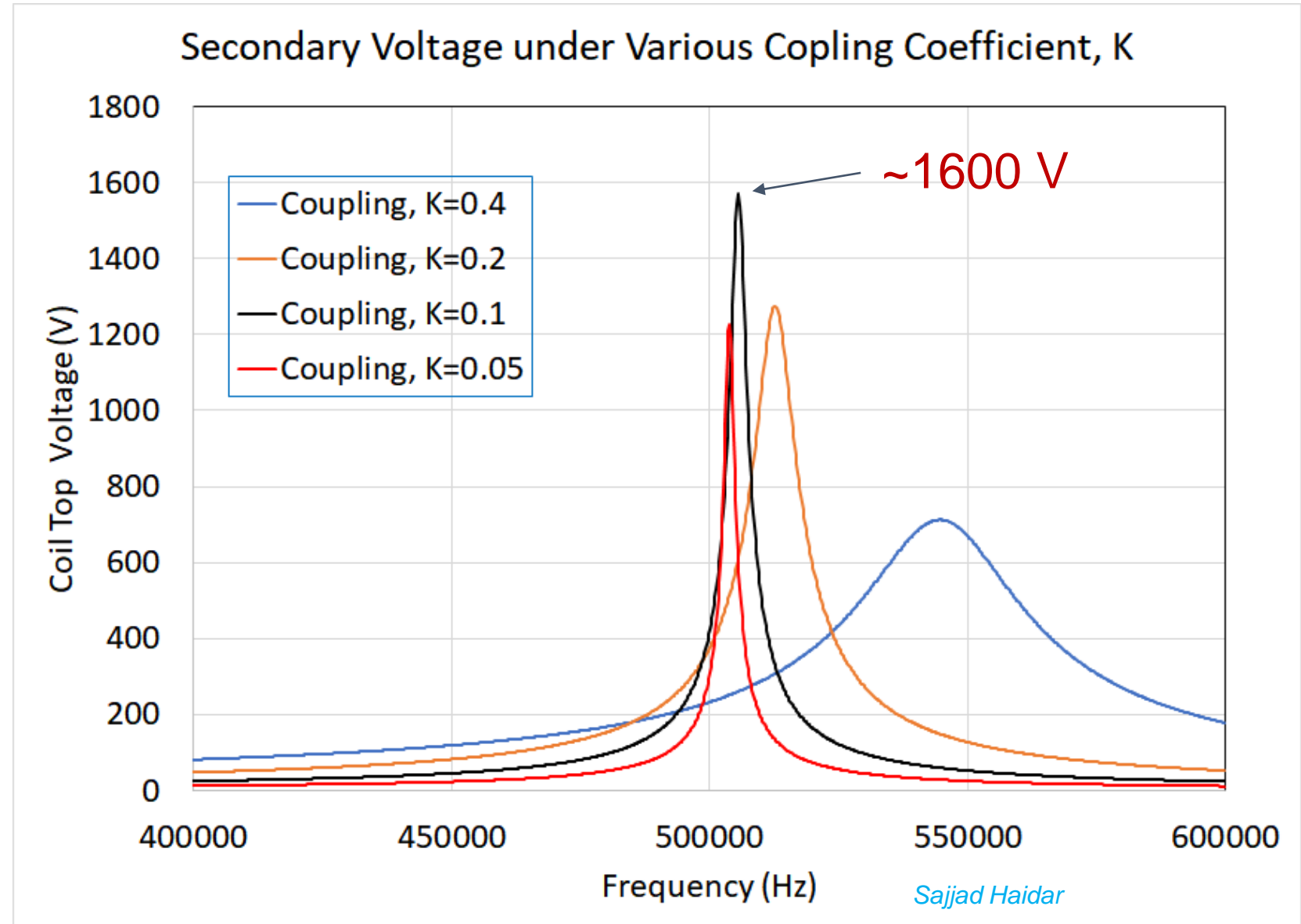For a loose Coupling: Very little energy is transferred to the secondary




Important Points to Note

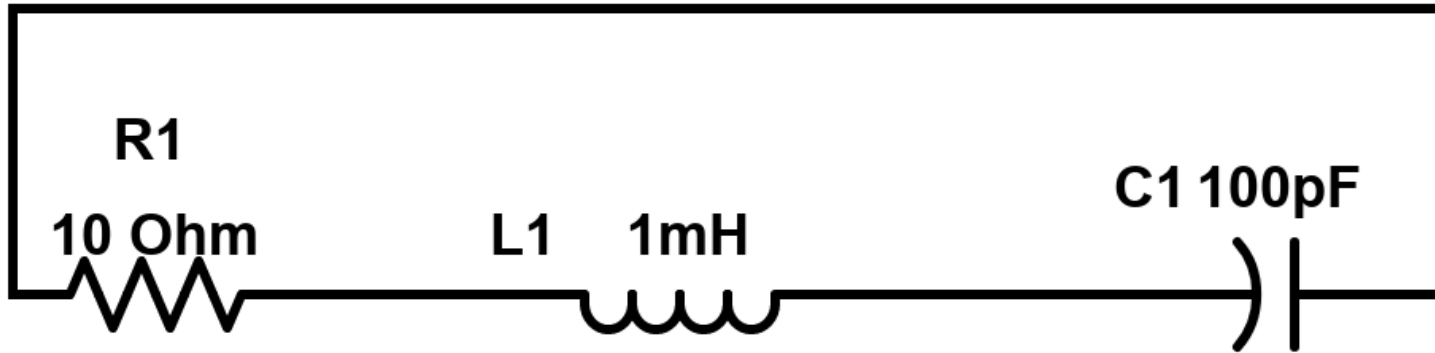

At resonant frequency (~505 kHz), voltage across Capacitor reaches ~1600 V. However, the source is only 10 V


V_c = 1600 V

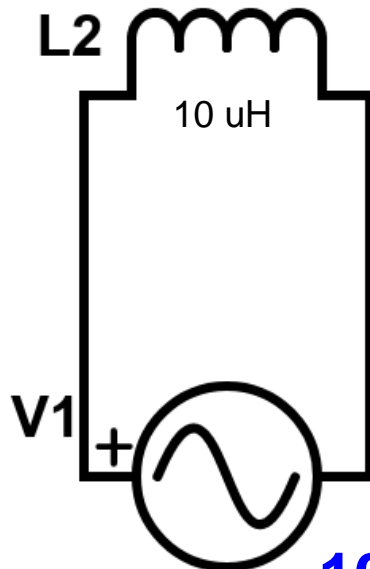

10V, 505 kHz


Voltage gain = 1600V/10V = 160

Tesla Coil as a Tuned LCR Circuit

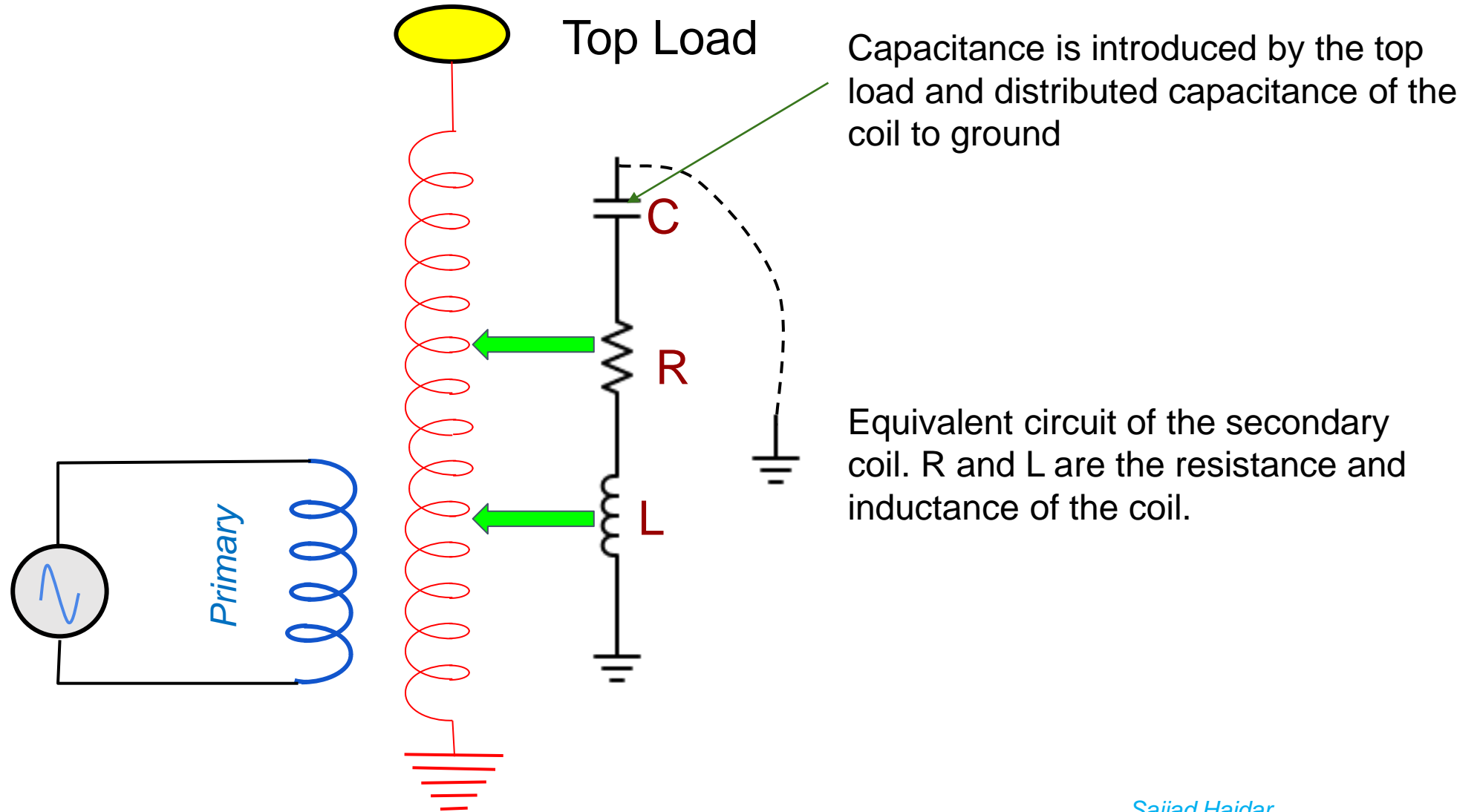


To Build a Successful Tesla Coil

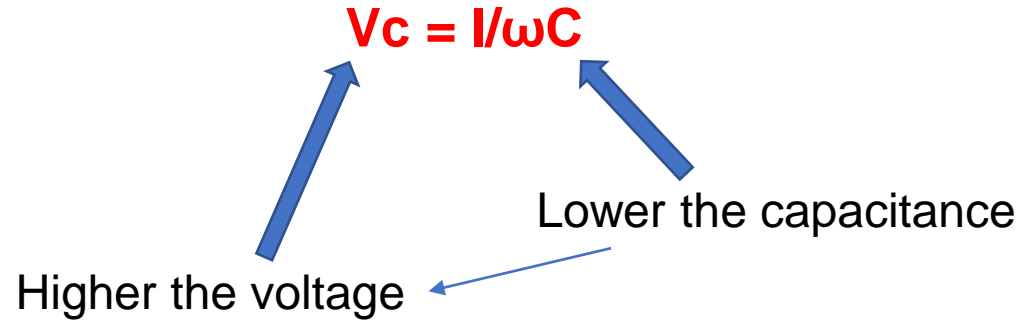1. Proper tuning to resonant frequency
2. Optimum Coupling (in our case , $K = 0.1$)
3. Low capacitance



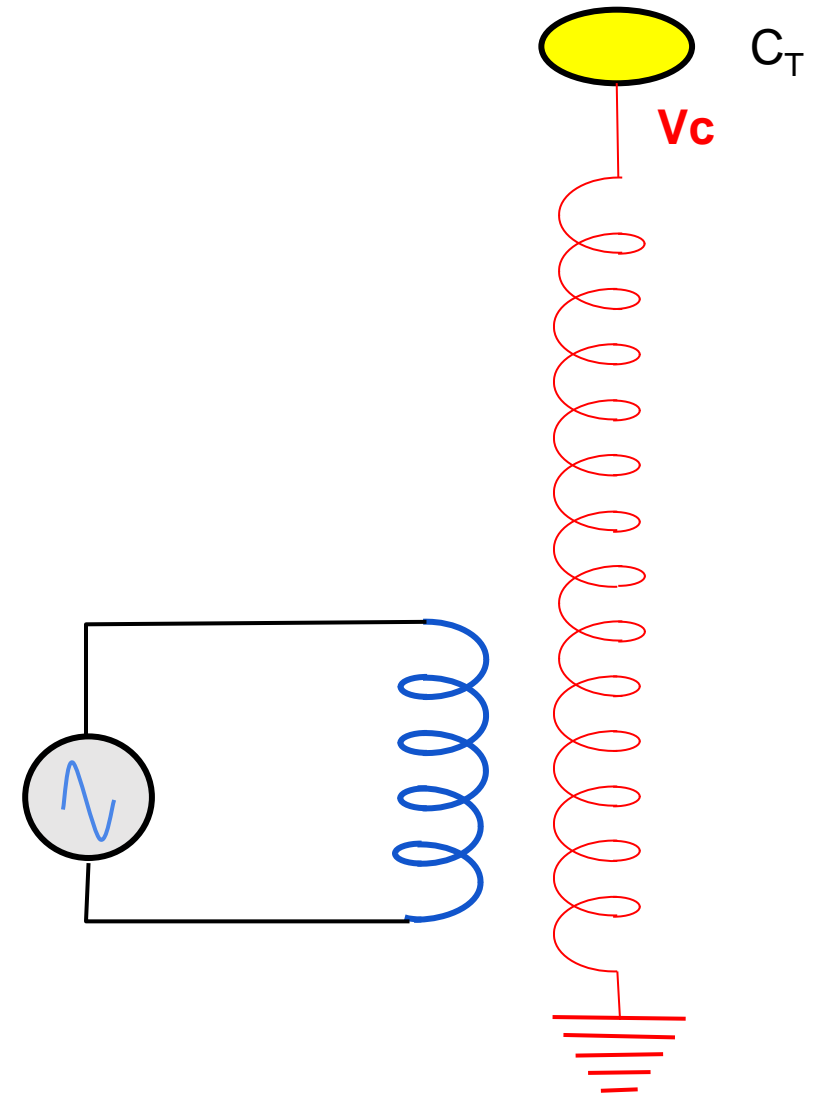4. If Top load is removed, capacitance will be lower. However, resonant frequency will go high. Component choice and tuning is more difficult. Power loss at the switching device will go higher.



Primary Coil Construction



Primary Coil: Conical

Number of Turns, $N=6$

Wire Gauge: AWG #8

Larger diameter: 23.5 cm


Smaller diameter: 19 cm

Width: 11 cm


Calculated inductance: ~ 8.1 uH


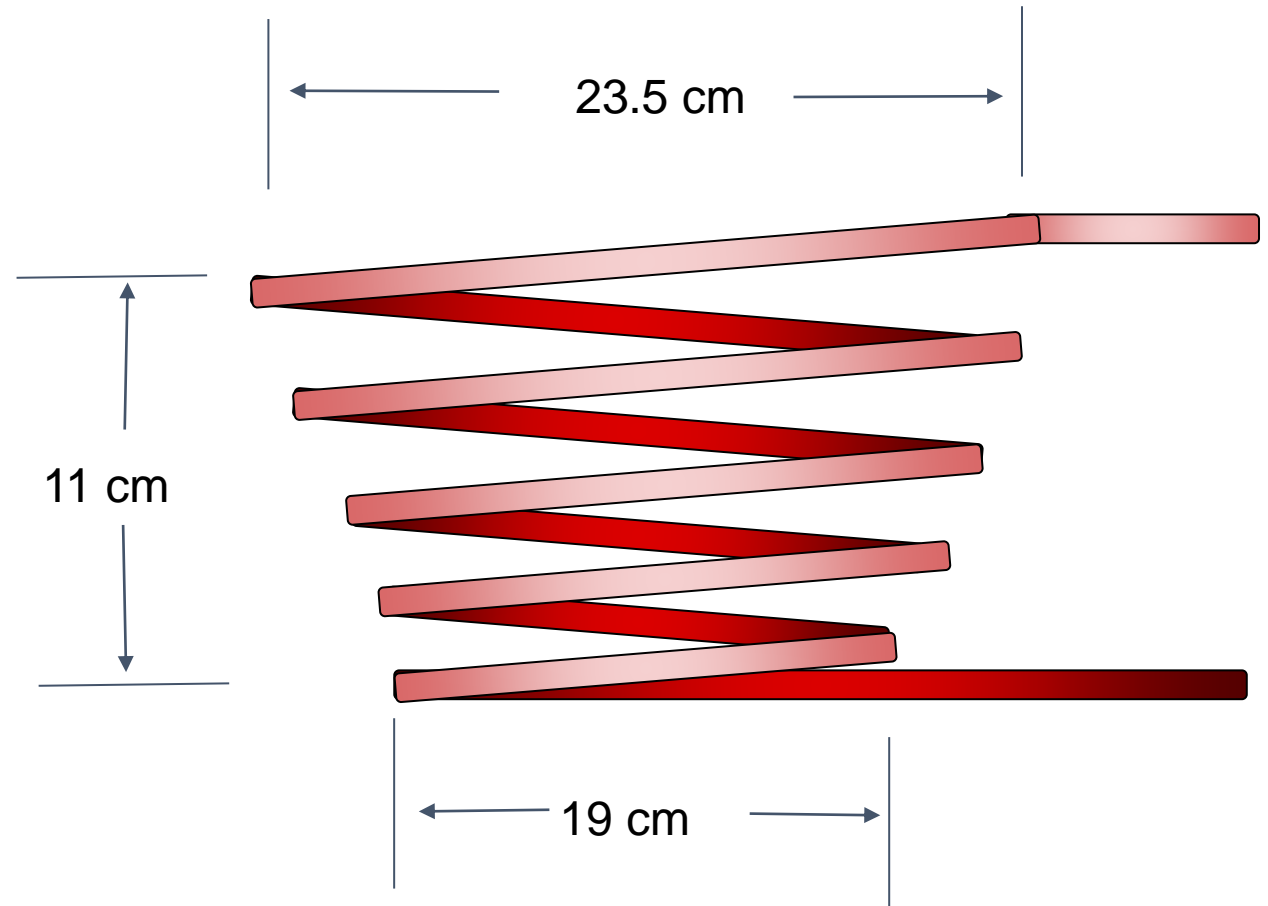
<https://coil32.net/online-calculators/conical-tesla-coil.html>



Primary Coil Construction

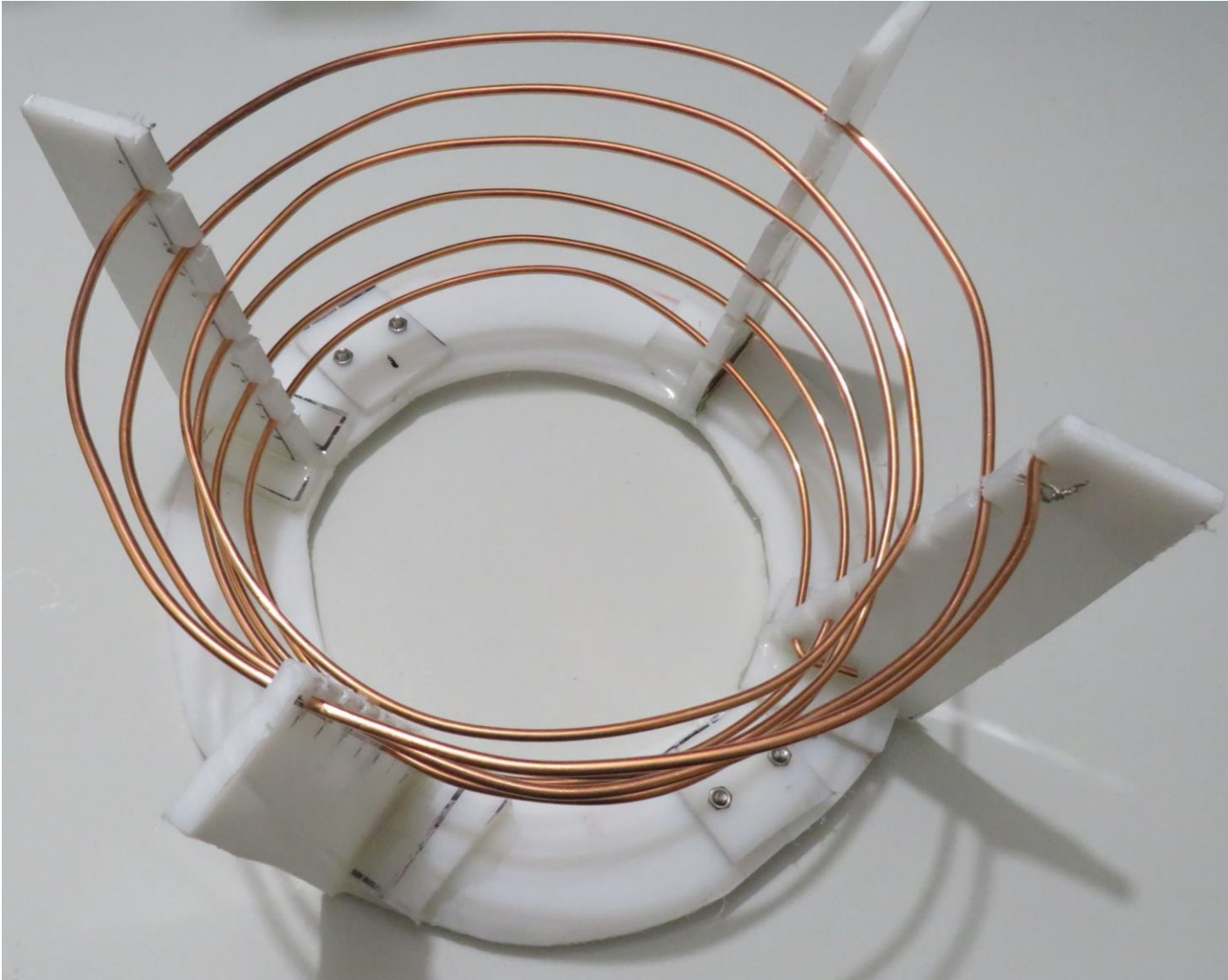

White acrylic sheet was used to make the coil format.

A jigsaw was used to cut the shapes and two-part epoxy was used to join the parts.

Parts Used for Secondary Coil

These parts are bought from local hardware store (Homedepot)



3" x 2" ABS Reducing Coupling



1.5" x 0.75" Bushing Adapter



4"X3" Adjustable Closet Flange Hub


As a coil Base



ABS PIPE 3 inches x 3 ft CELL CORE

Copper wire is wound on this pipe

Secondary Coil Construction

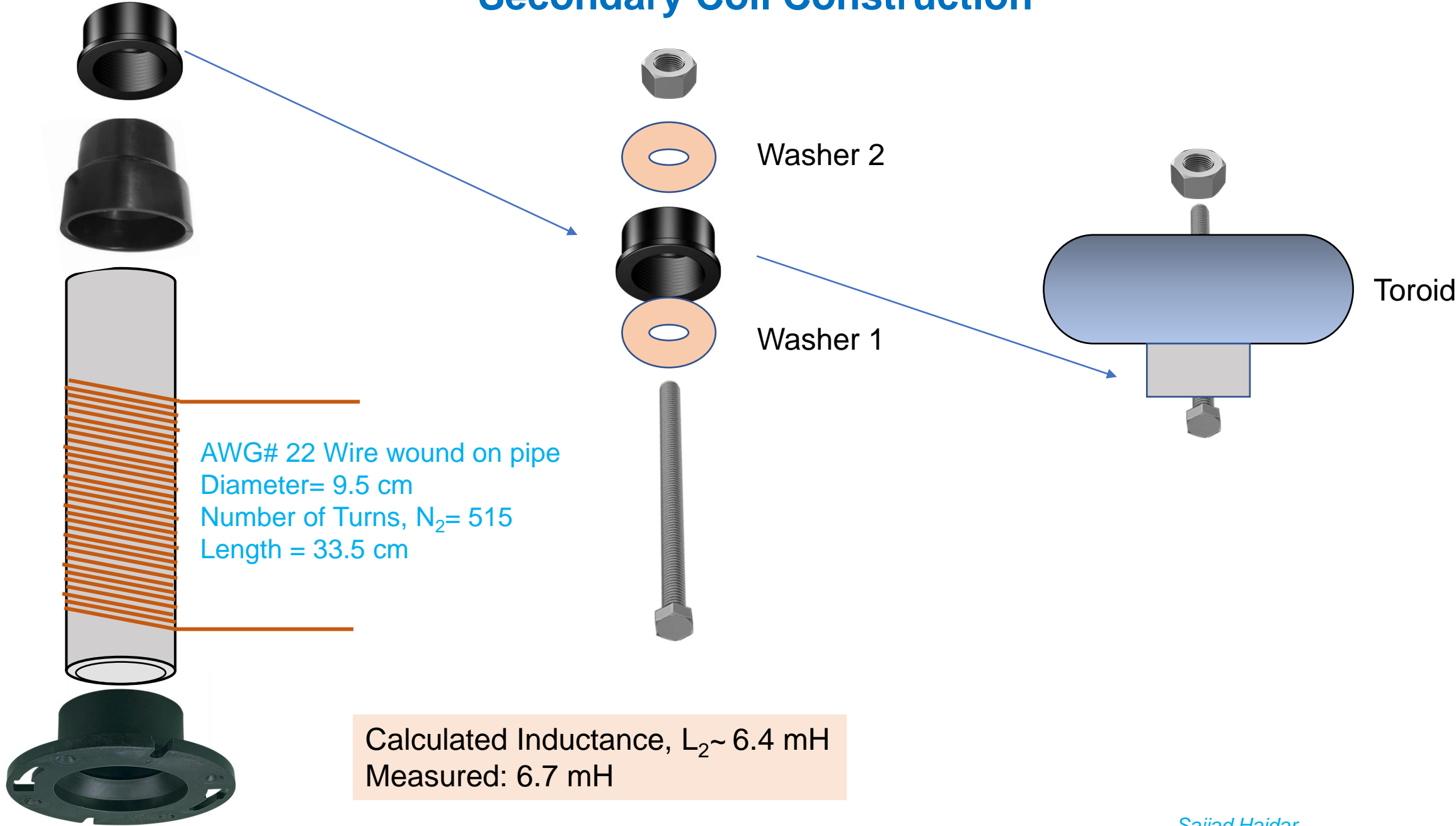

Primary and Secondary Coil-Data at a Glance

Secondary Coil:

New Tesla coil Data:

Coil Dimension: Diameter: 8.95 cm (3.5 inches), Length: 33.5 cm (13.2 inches)

Wire Gauge: AWG# 22, Number of Turns, $N = 515$

$R = 13.5 \text{ Ohm}$

$L = 6.7 \text{ mH}$

Considering the top capacitance, resonant frequency: 460kHz

Capacitance: $\sim 18 \text{ pF}$

Primary Coil: Conical

Number of Turns, $N = 6$

Larger diameter: 23.5 cm

Smaller diameter: 19 cm


Width: 11 cm

Calculated inductance: 8.1 uH

Secondary Coil and Tesla Coil Base




Equivalent Circuit

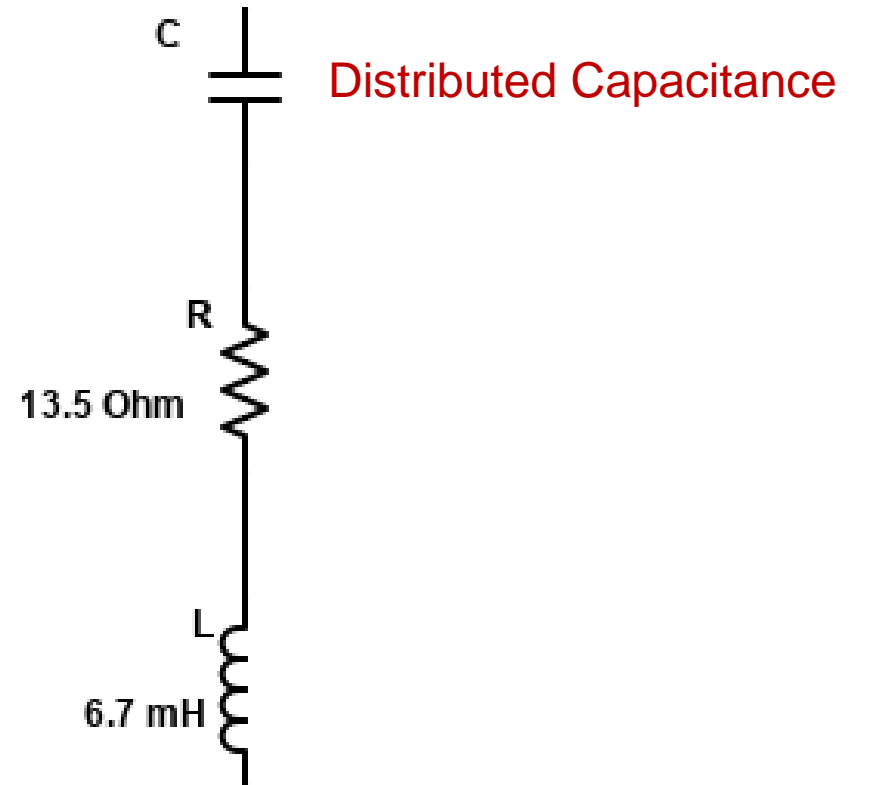

Calculated Inductance, $L_2 \sim 6.4$ mH
Measured: 6.7 mH

Tesla Secondary Coil : Photo

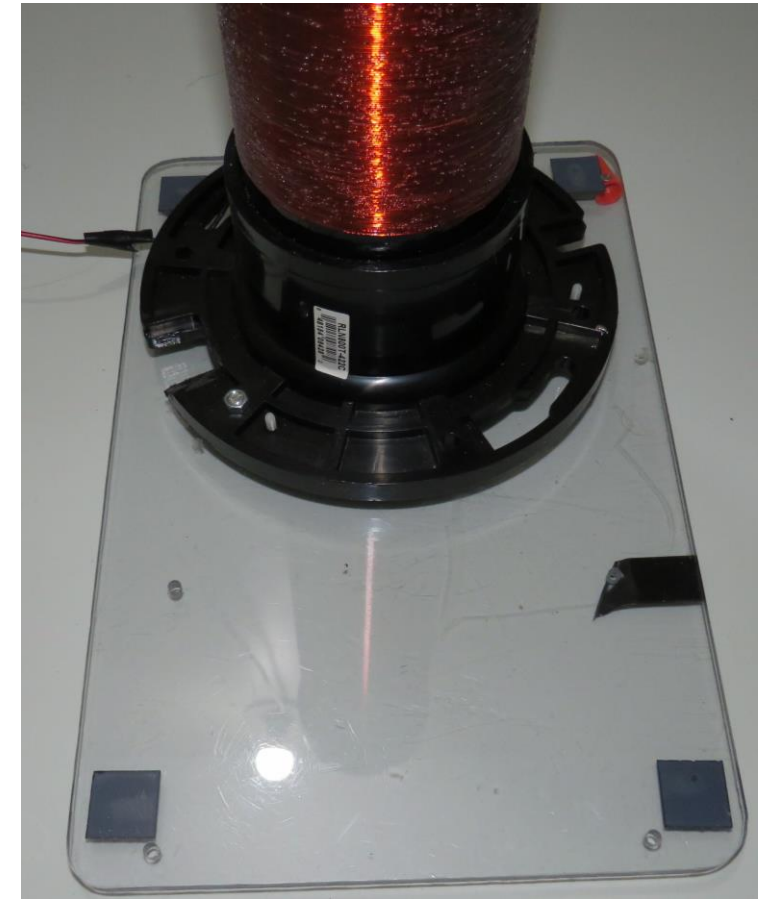

Coil-base on a plexiglass plate

Sajjad Haidar

Top Load Construction

Flexible Aluminum Duct: 3 inch x8 foot (Expanded)



Bent to form toroid
Aluminum sheet-disc
And foil tape is used



Calculating the capacitance of a toroid:

D1: the major diameter of the
D2: is the minor diameter of the ring of the toroid.

$$D1 = 9.5''$$

$$D2 = 3''$$

This formula is using inches for measurements. Result is in pF.

$$C = 2.8 \cdot \left(1.2781 - \frac{D2}{D1}\right) \cdot \sqrt{\frac{2 \cdot \pi^2 \cdot (D1 - D2) \cdot \left(\frac{D2}{2}\right)}{4 \cdot \pi}}$$

$$C \sim 10.5 \text{ pF}$$



Sajjad Haidar



Tesla Coil with Top Load

Calculated top load capacitance:
 $C_T = 10.5 \text{ pF}$

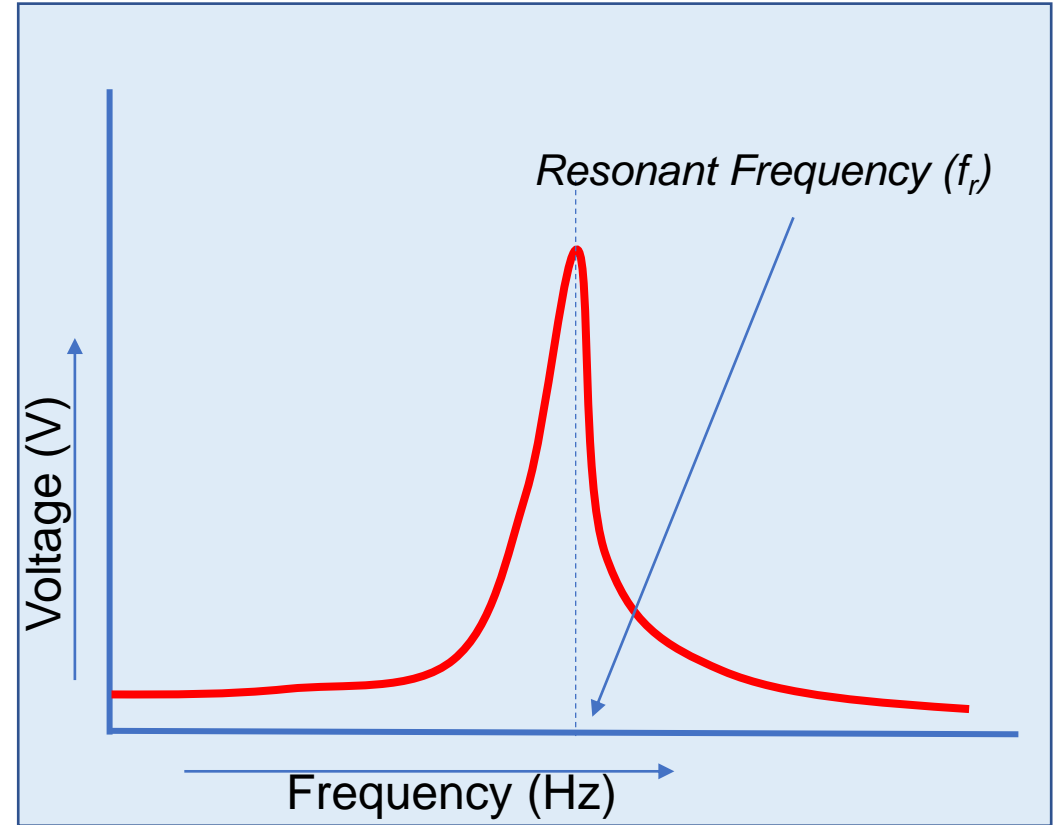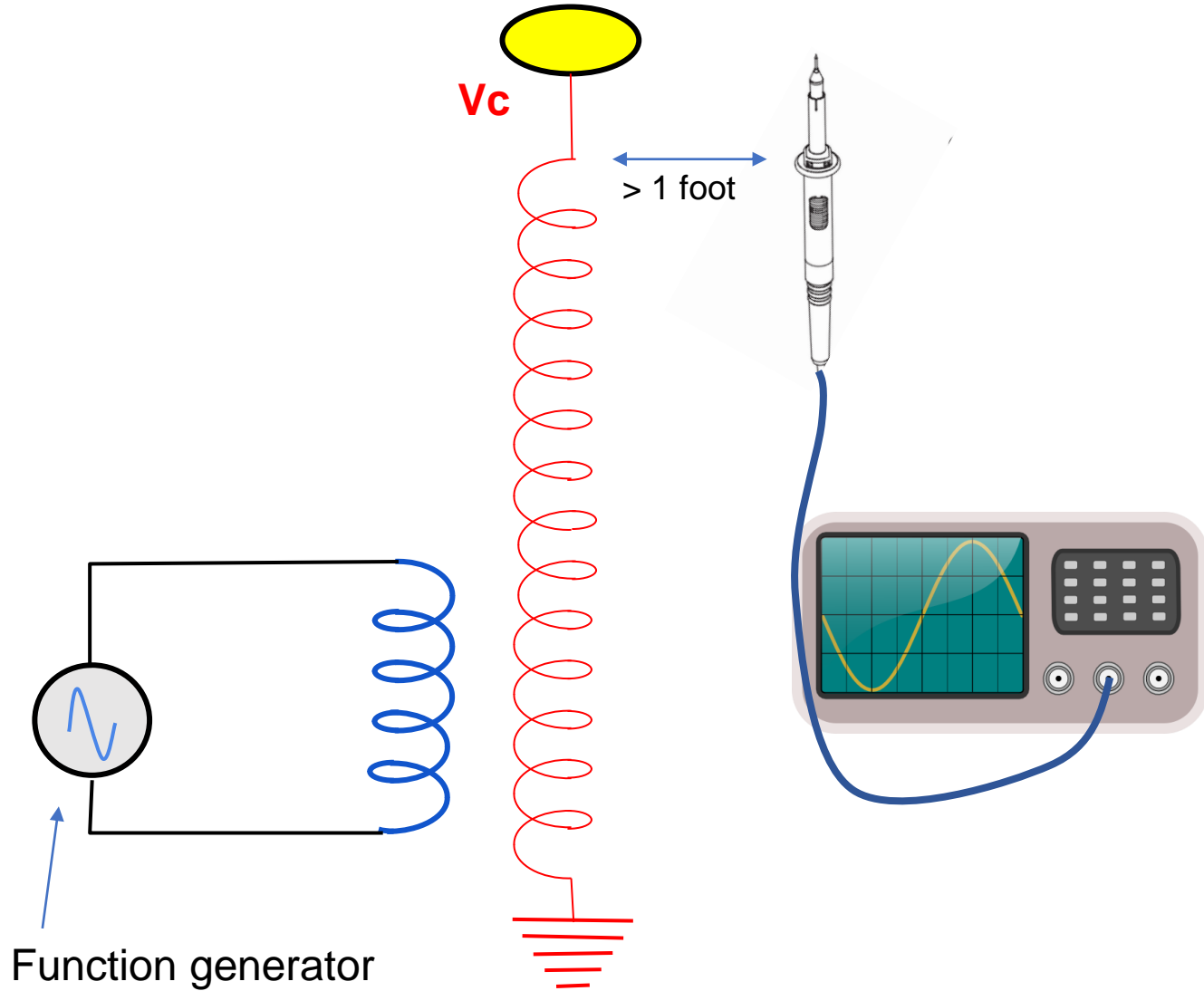Experimental Determination of Resonant Frequency



Experimental Setup to Determine the Resonance-Frequency

Resonant frequency found: 460 kHz

Inductance of the secondary coil: 6.7 mH


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$



Which gives, $C \sim 18 \text{ pF}$

Distributed capacitance of the coil:

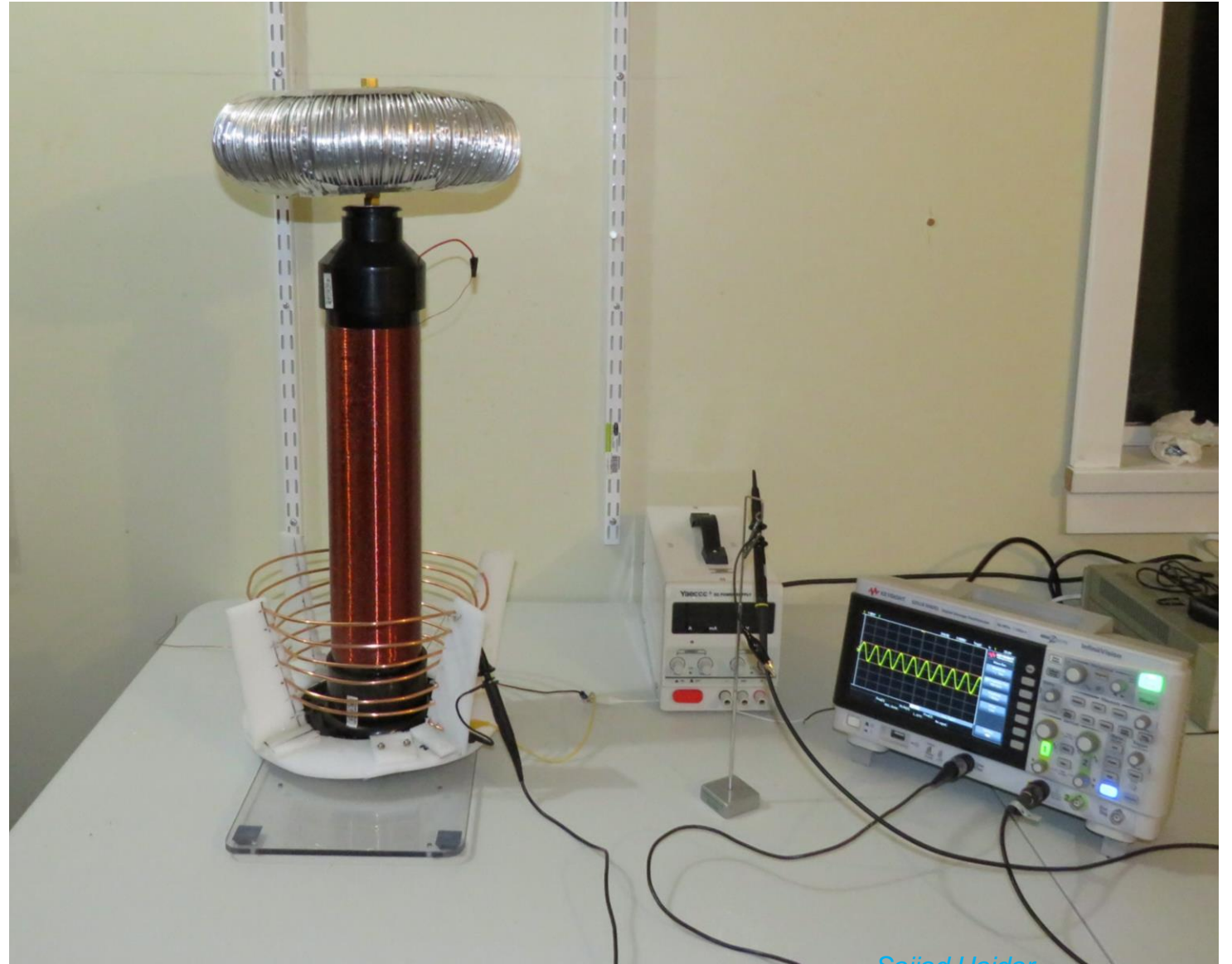
$$C_D = C - C_T = 18 - 10.5 = 7.5 \text{ pF}$$



Equivalent Circuit Simulation in LTSpice

Primary inductance, $L1 = 8 \mu\text{H}$ + connecting wire inductance $\sim 2 \mu\text{H}$, $L1 \sim 10 \mu\text{H}$

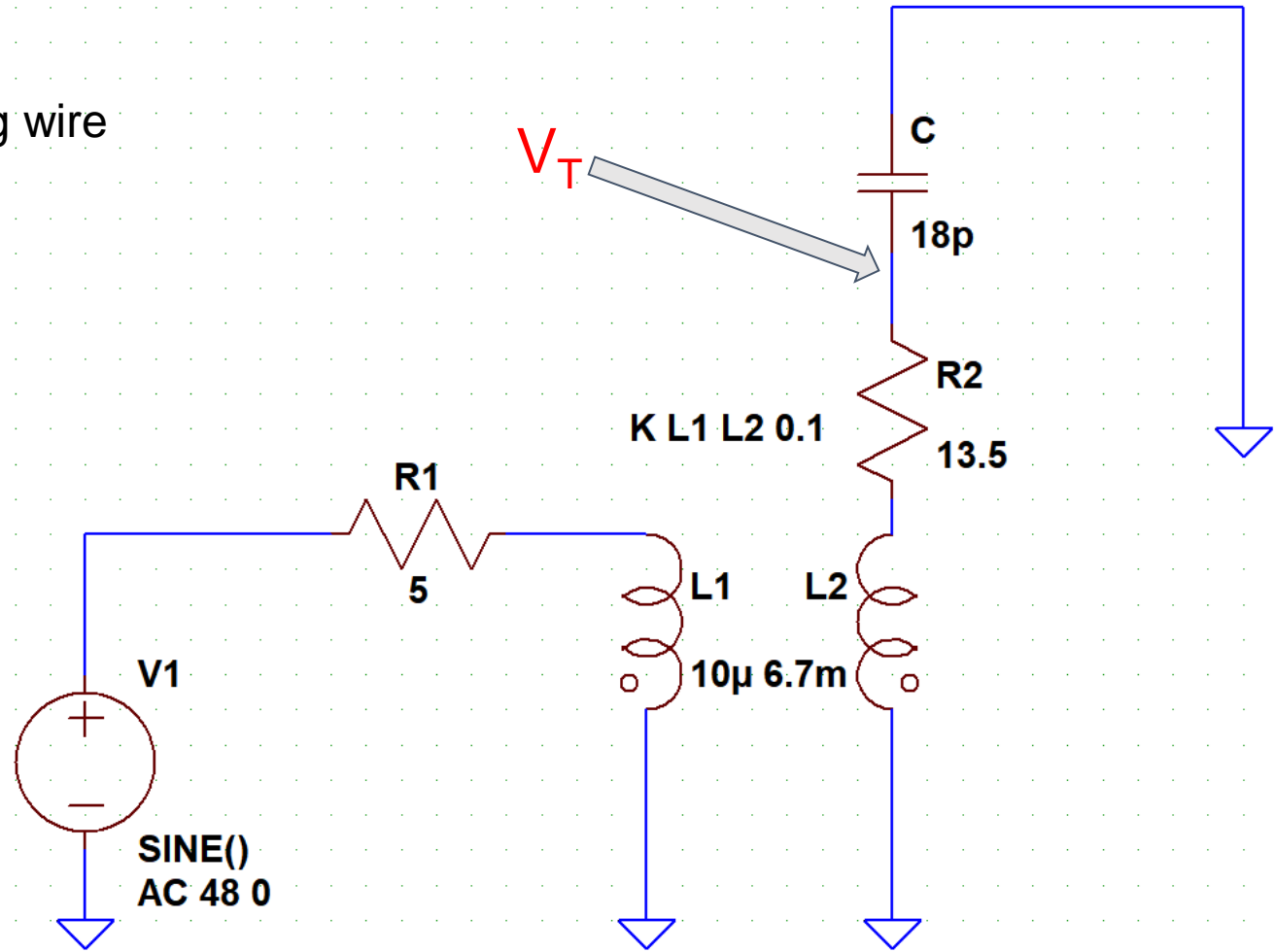To protect the main switching circuit (MOSFET) a series resistance ($\sim 5 \text{ Ohm}$) is used. $R1 \sim 5$



Simulation Result

Voltage gain




47 kV


48 V




~1000

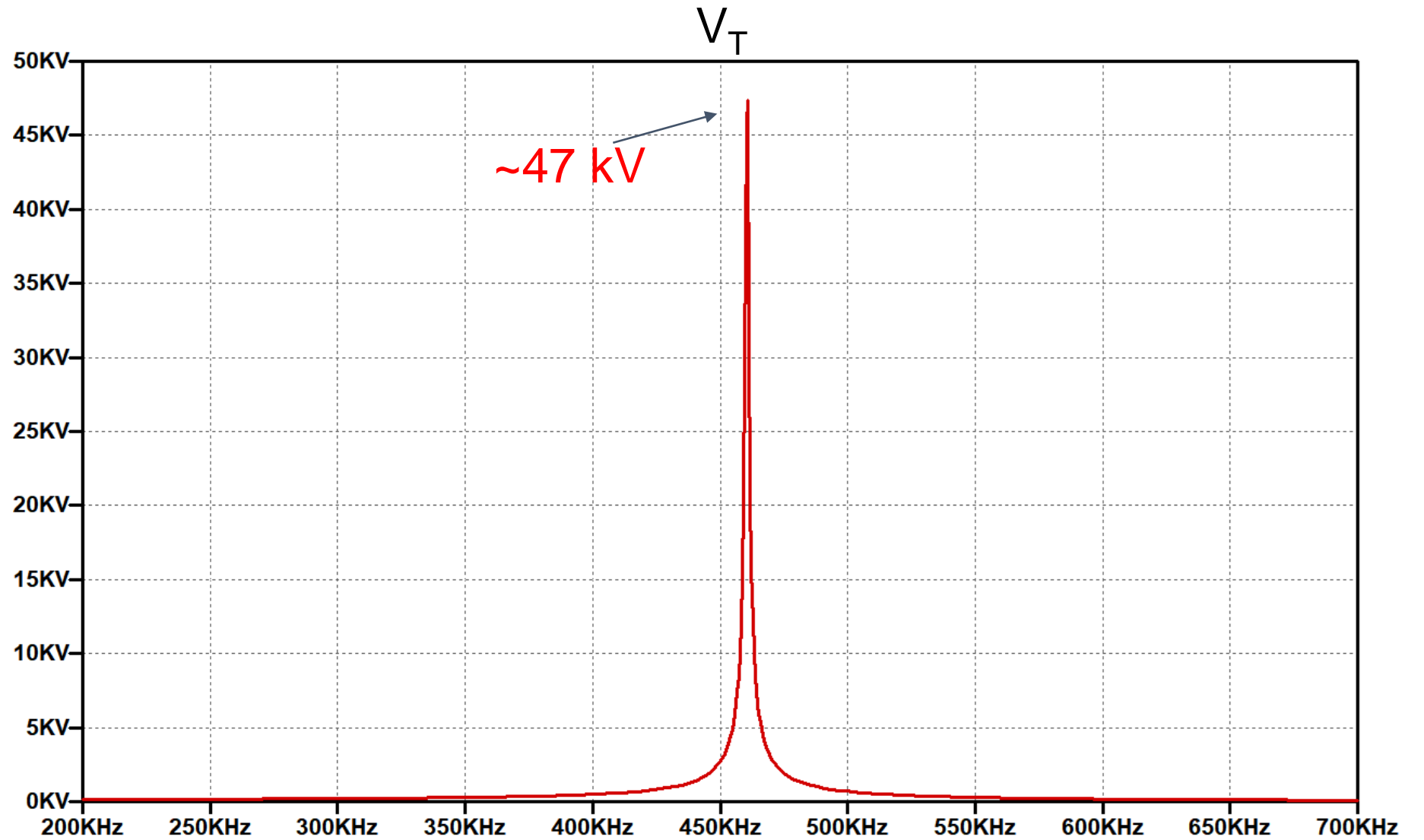



Practical Tesla Coil Driver Circuits

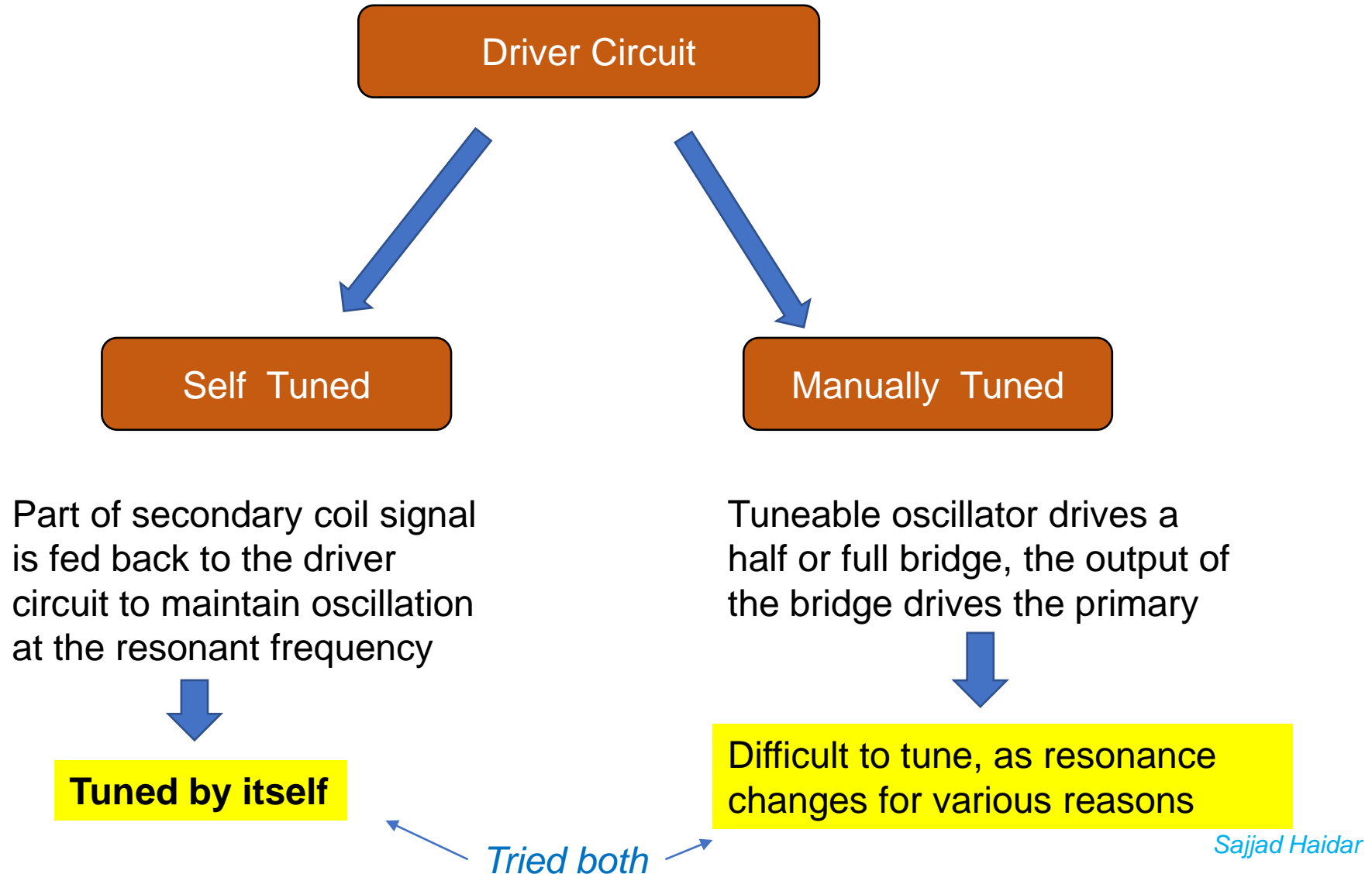

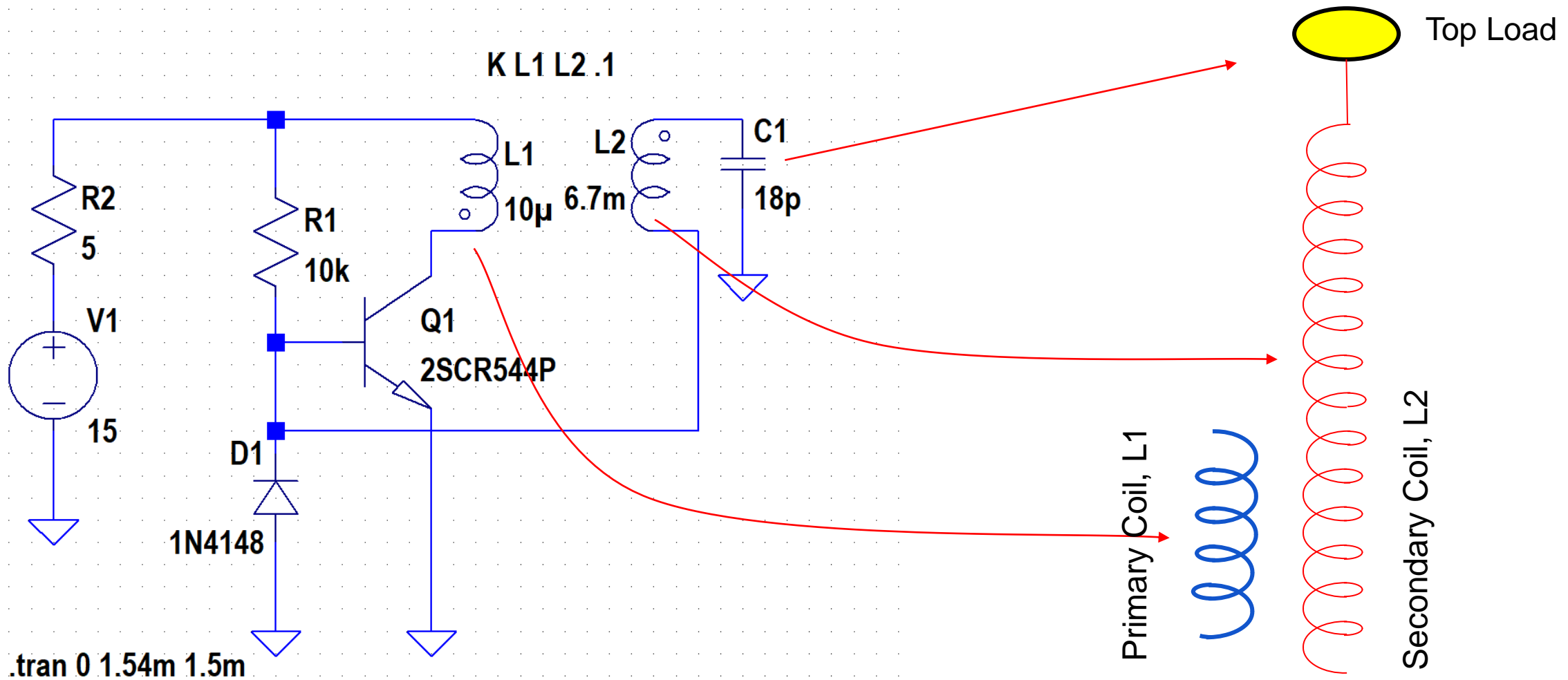
Simulation: Simple Slayer Exciter Circuit to Test the Tesla Coil



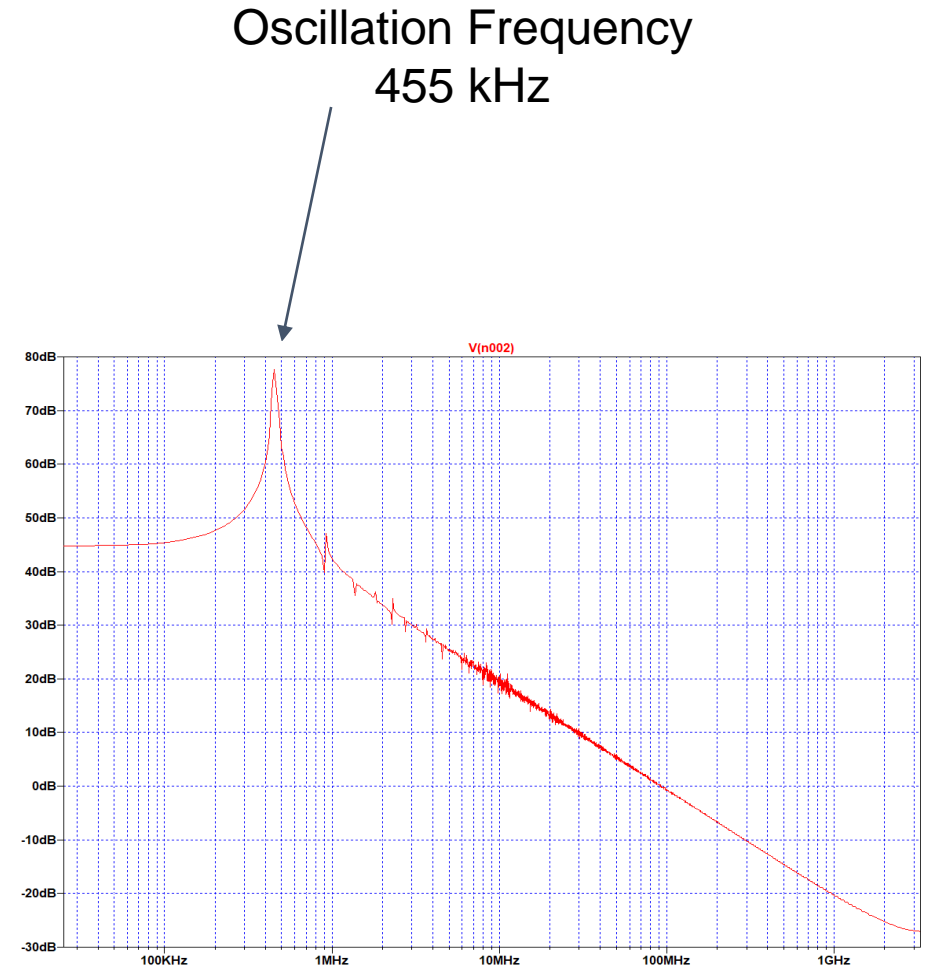
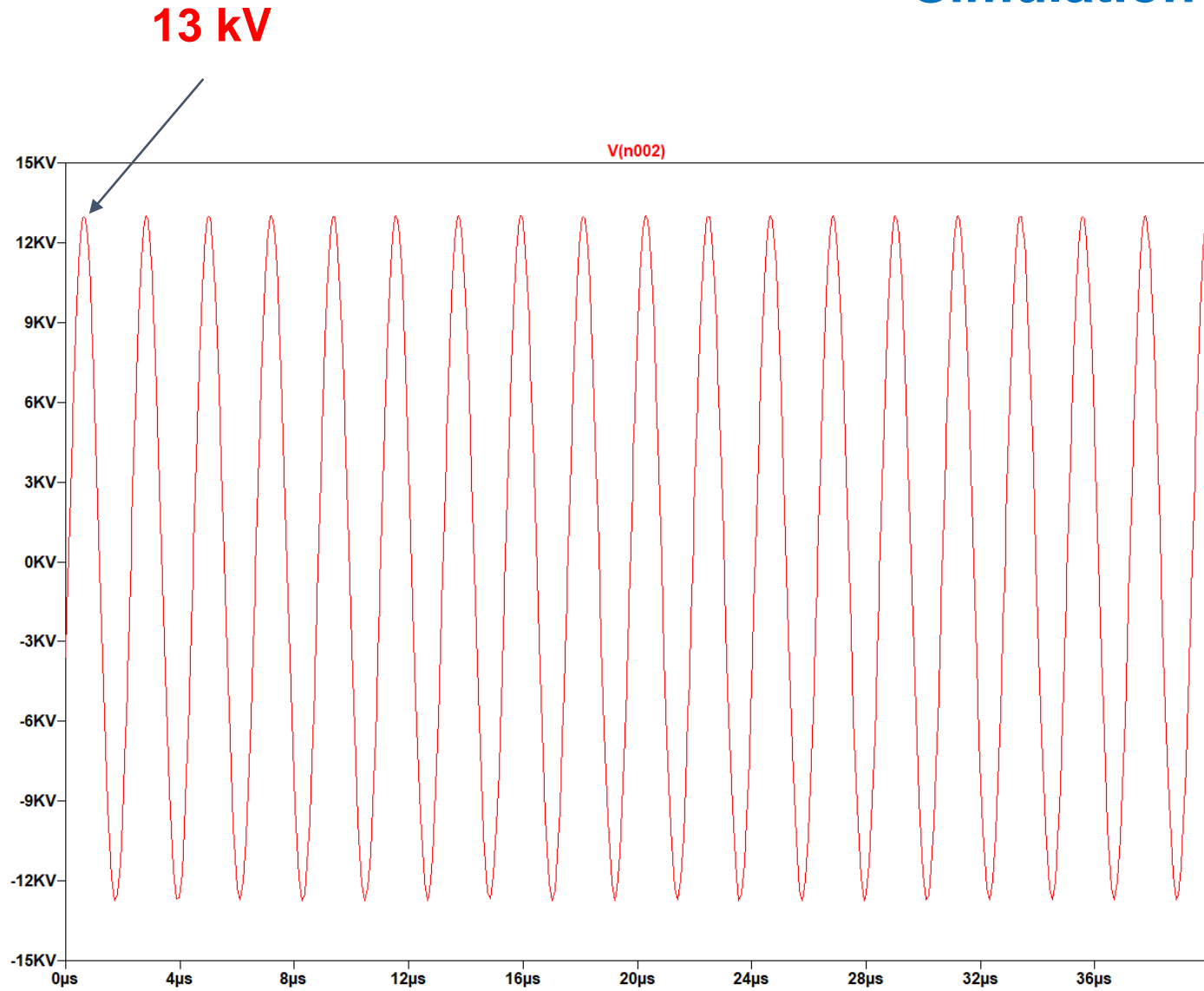
Simple Slayer Exciter Circuit to Test the Tesla Coil Simulation Result



Simulated Tesla Coil Voltage

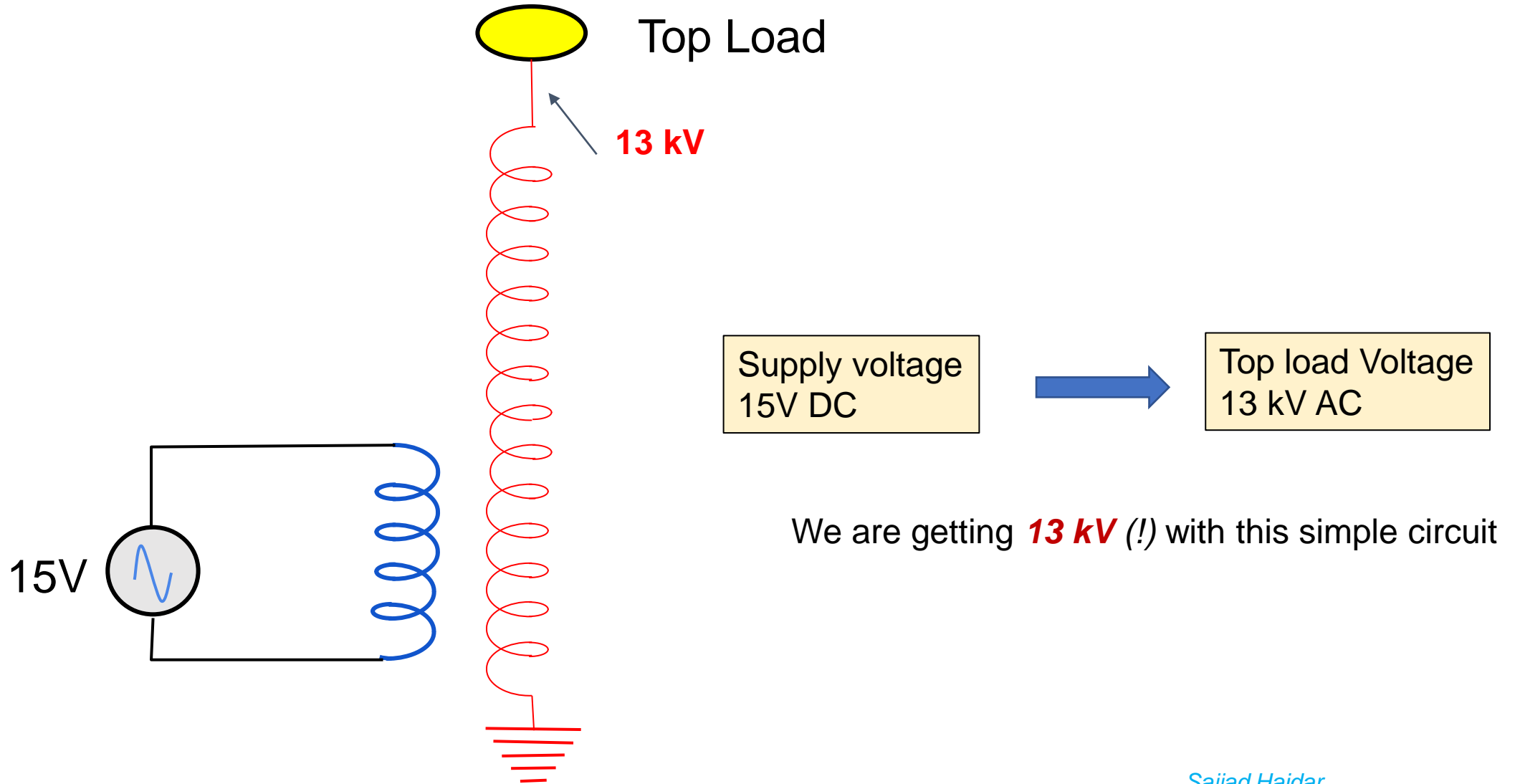

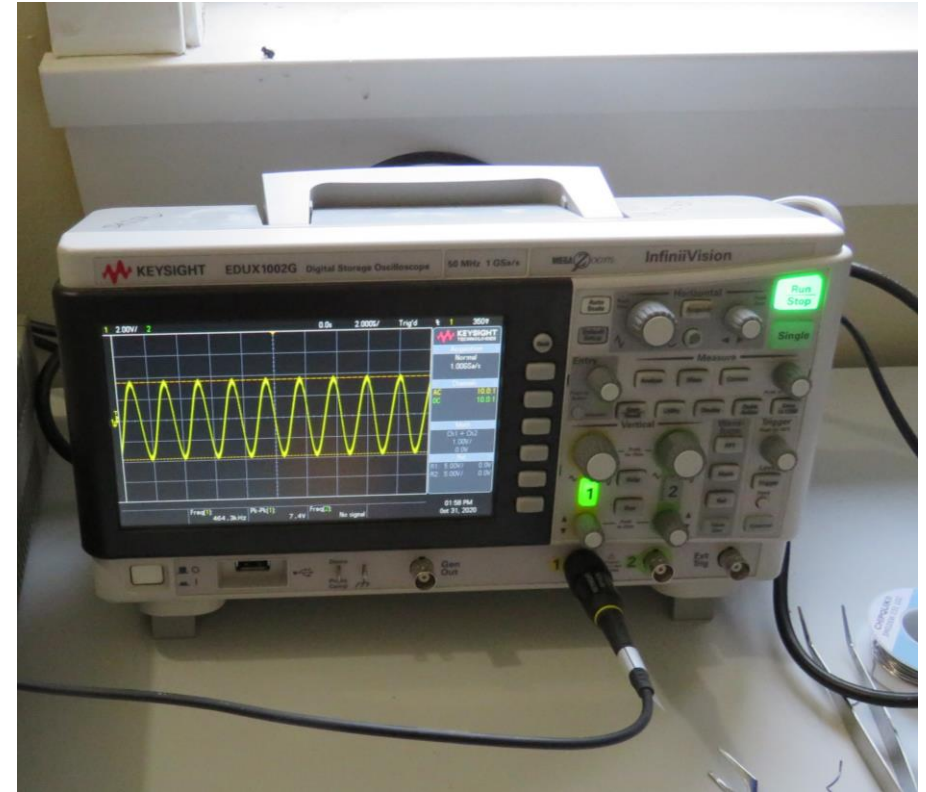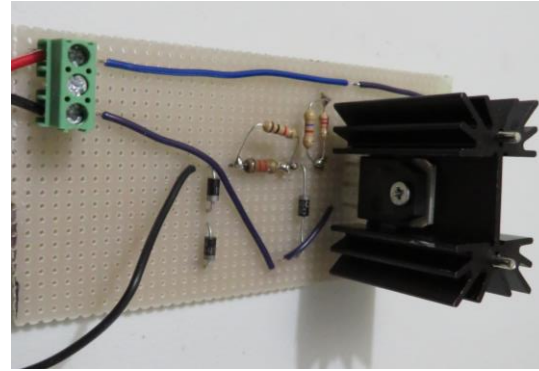
Test of the Simple Slayer Exciter Circuit



Sajjad Haidar



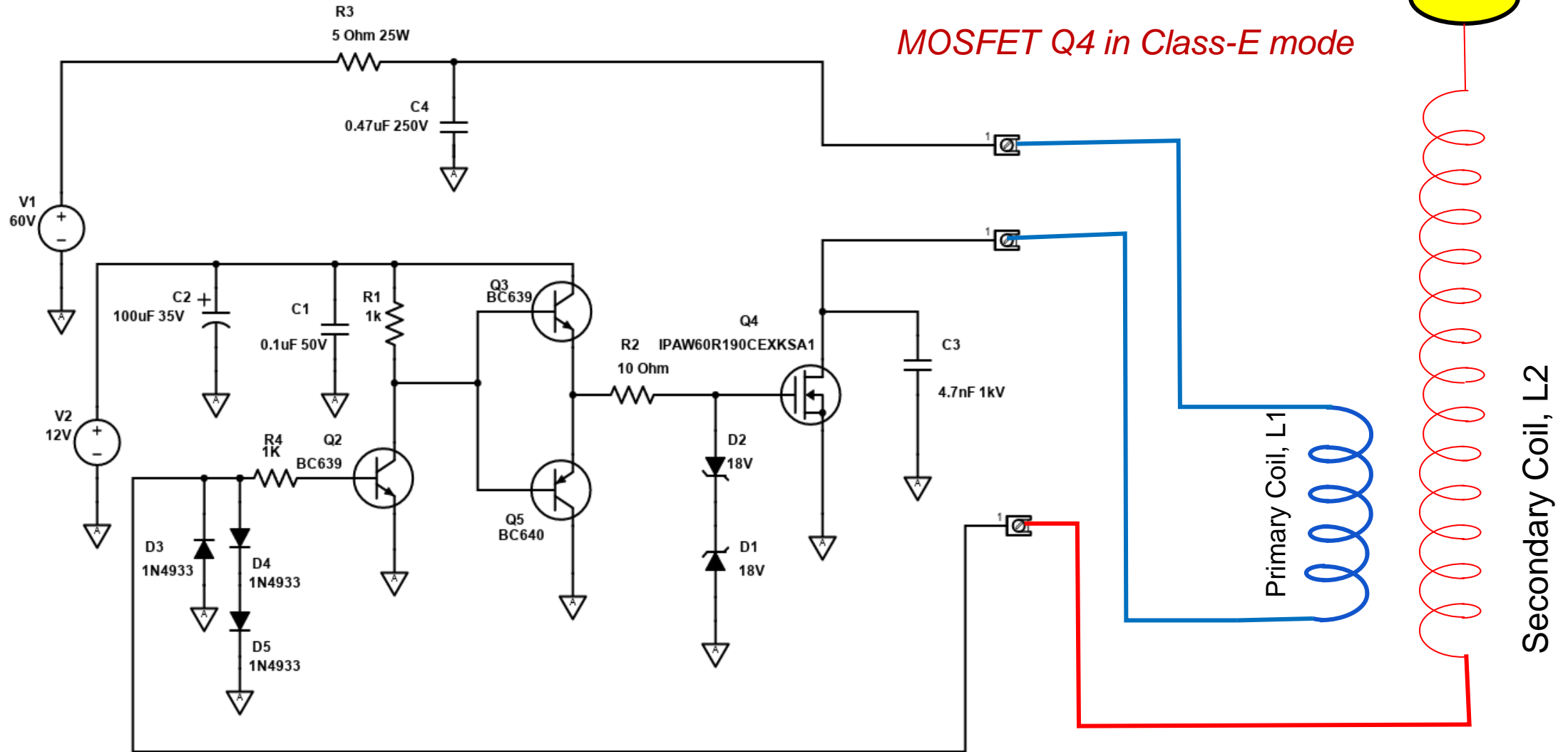To Achieve Higher Voltage (Bigger Arc) Modified Circuit is Used





MOSFET Q4 in Class-E mode

Primary Coil, L1



Secondary Coil, L2

110V DC Power Supply for Tesla Coil

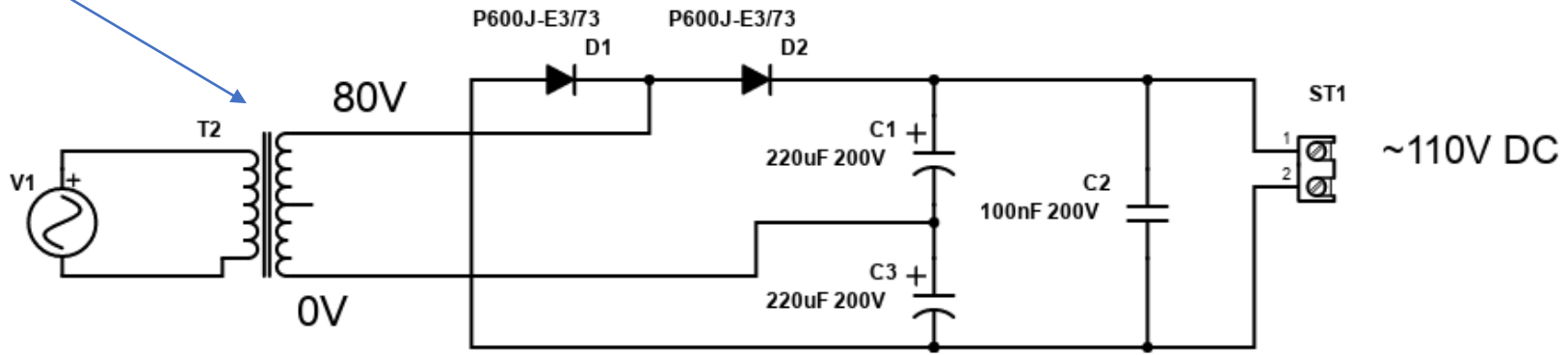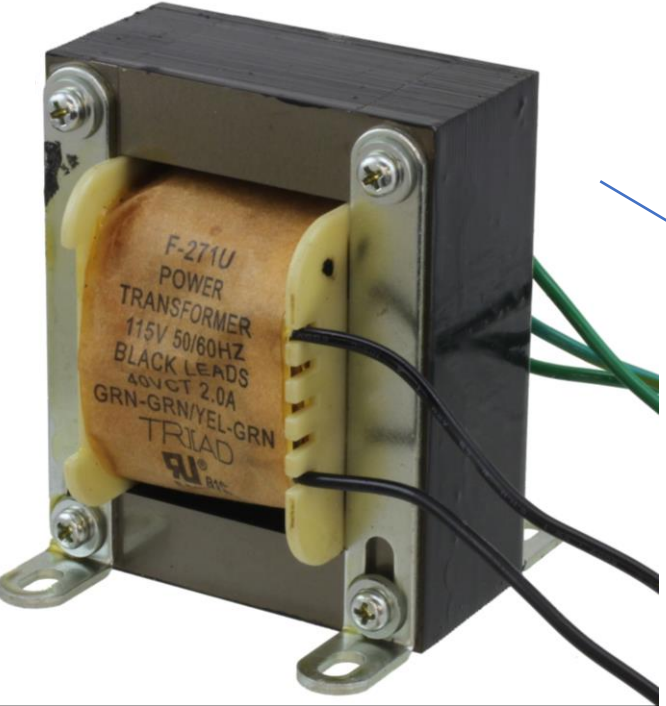


F-271U
Primary: 115V Ac
Secondary: CT, 40V, 2A
Power 80 VA

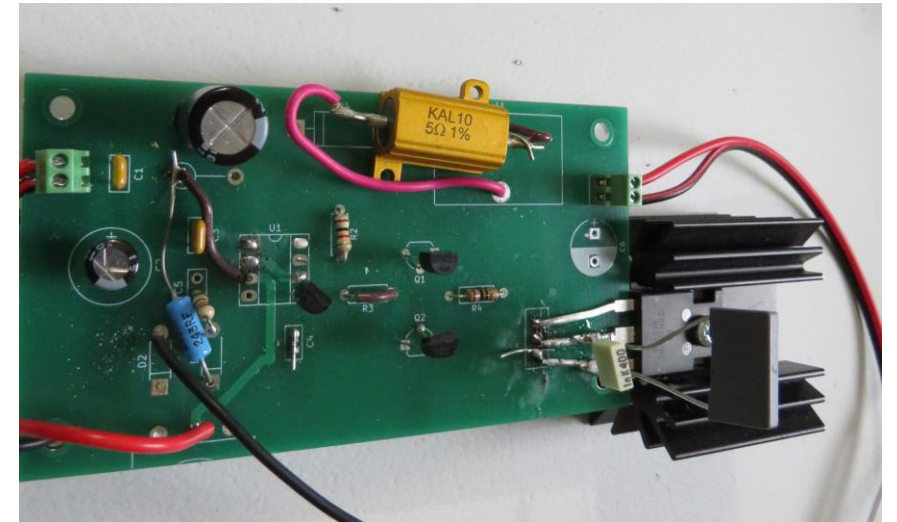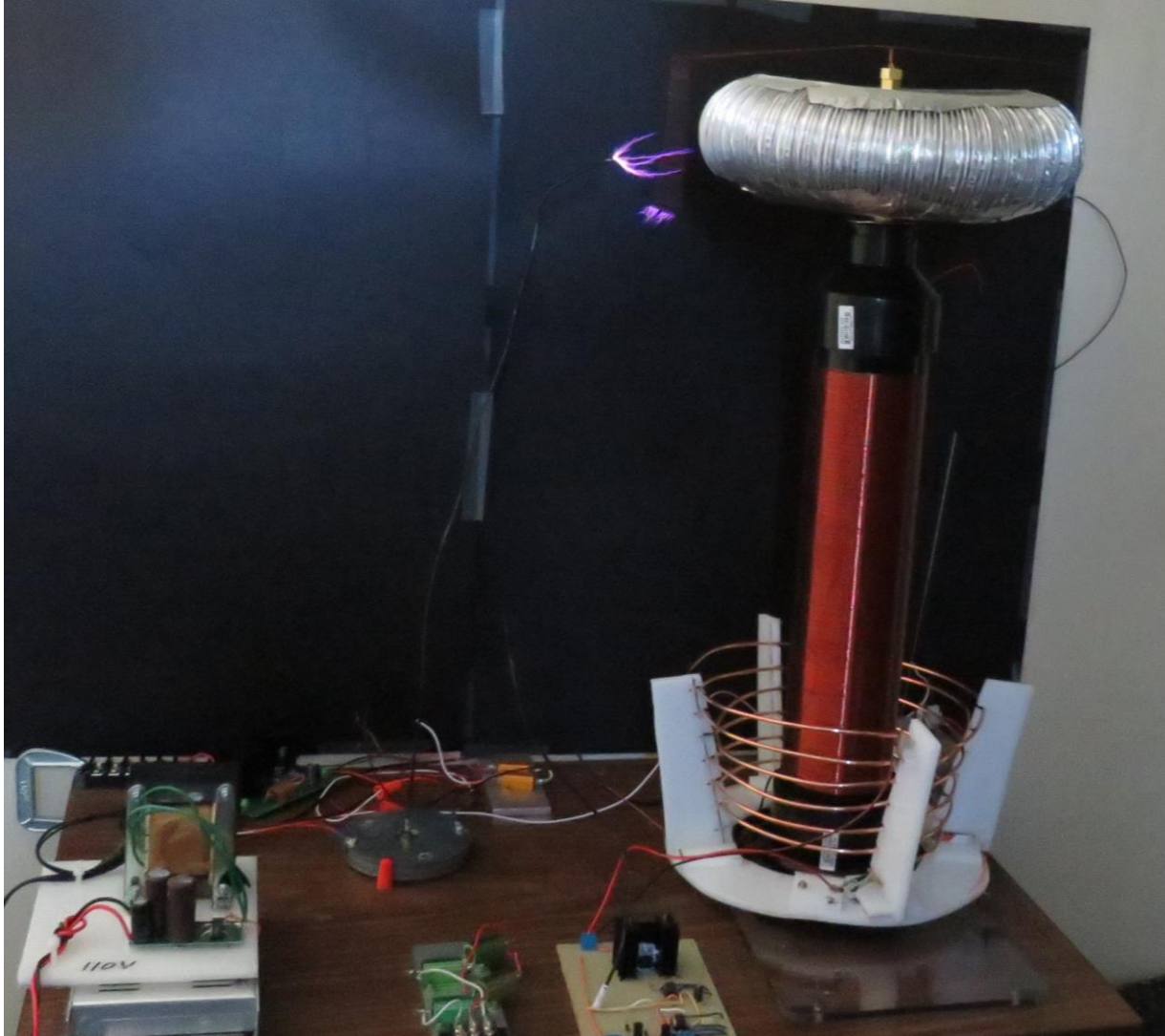Class-E MOSFET Slayer Exciter Circuit, Driving Voltage: 110V DC




Rotating Ionic Propulsion with Tesla Coil

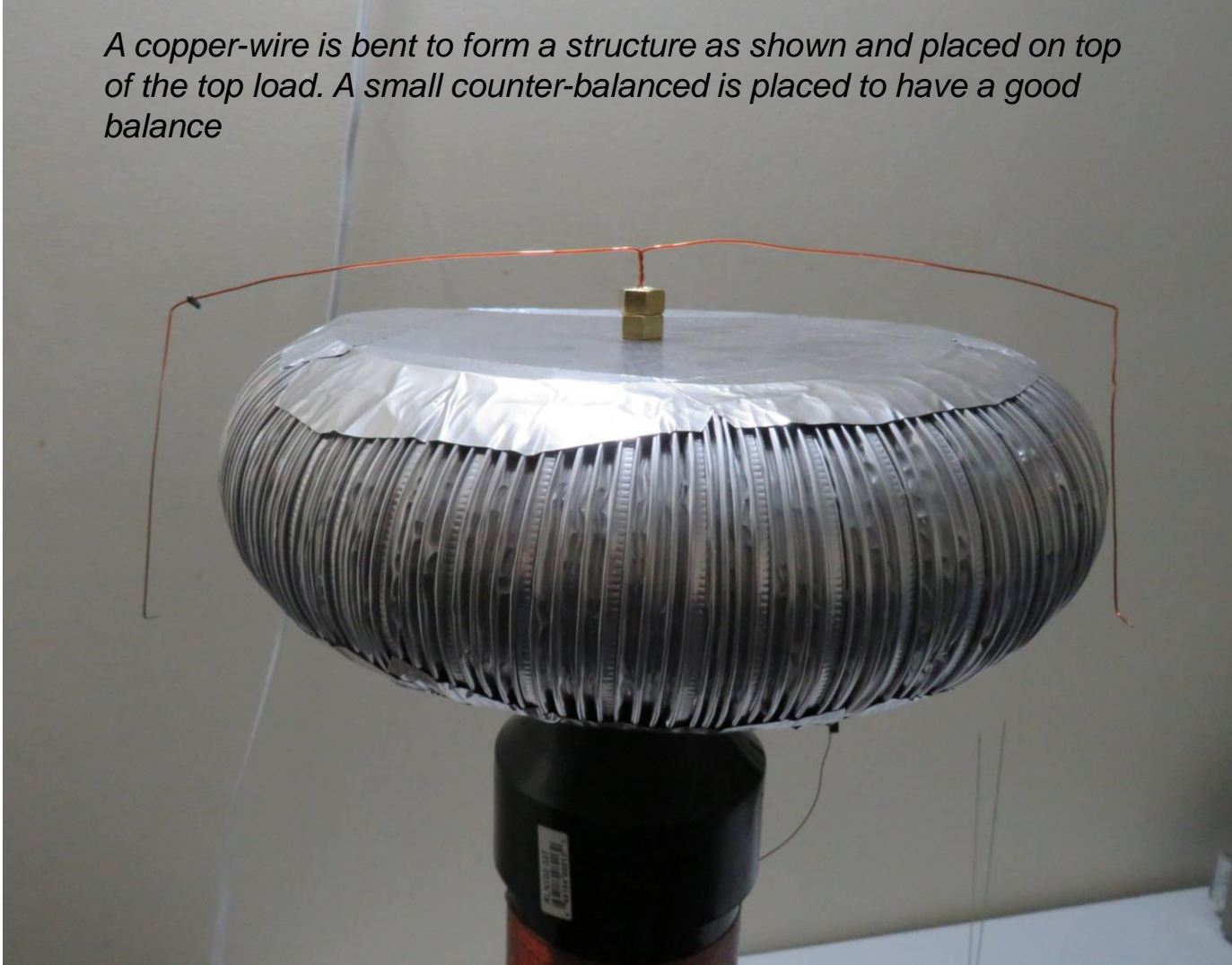A copper-wire is bent to form a structure as shown and placed on top of the top load. A small counter-balanced is placed to have a good balance


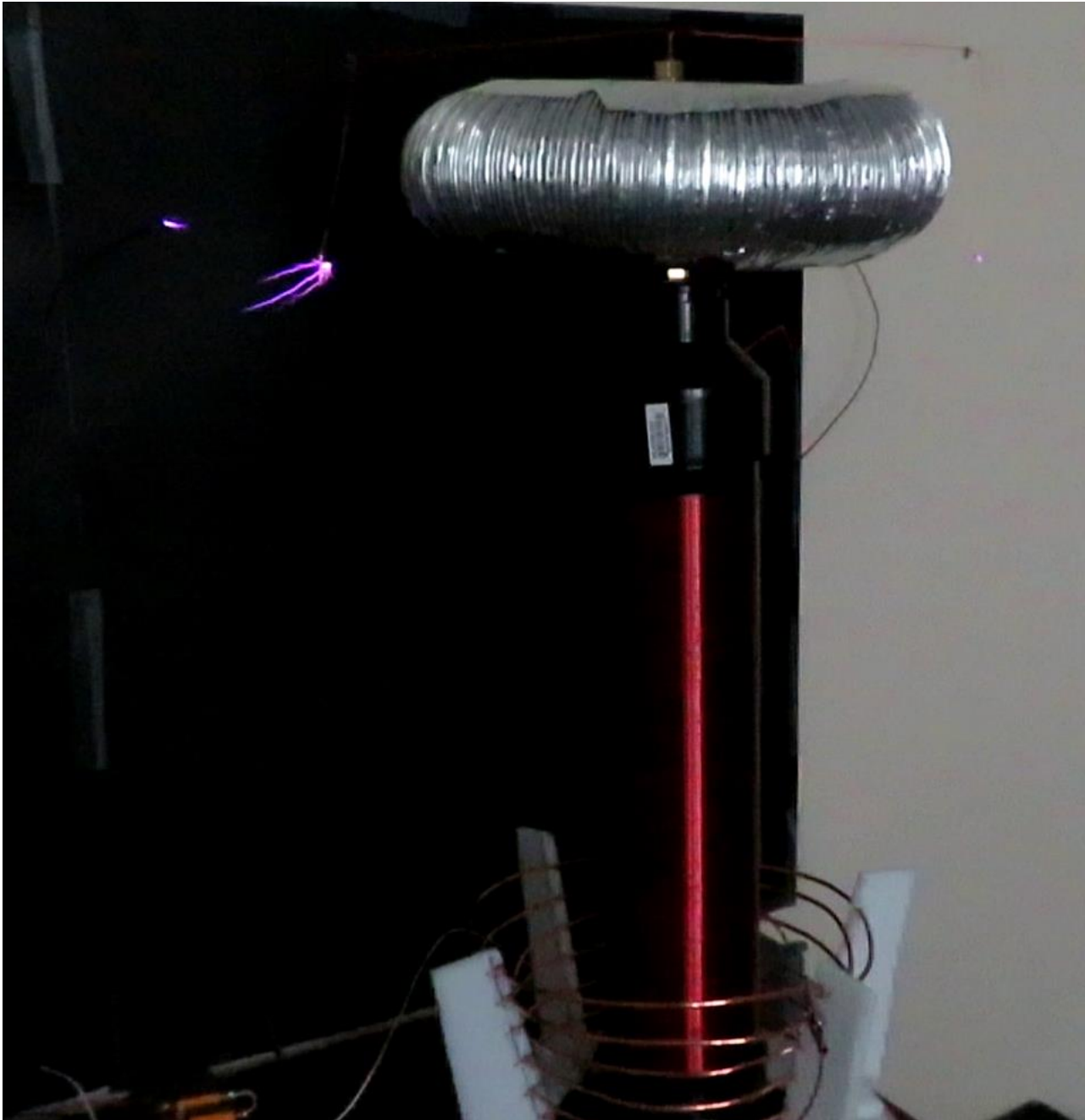
<https://www.youtube.com/watch?v=U2QSbAbUgPc&feature=youtu.be>



<https://www.youtube.com/watch?v=VQNjBilo0aY&feature=youtu.be>

Tesla Coil with Jacob's Ladder

A pair of steel-wire is bent as shown to form a Jacob's ladder. One terminal is connected to the ground and the other to the top load. Arcing starts from the bottom and reaches the top. Cycle begins



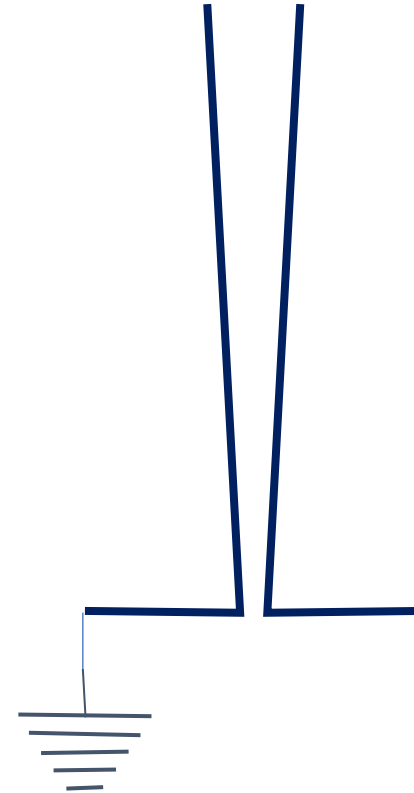
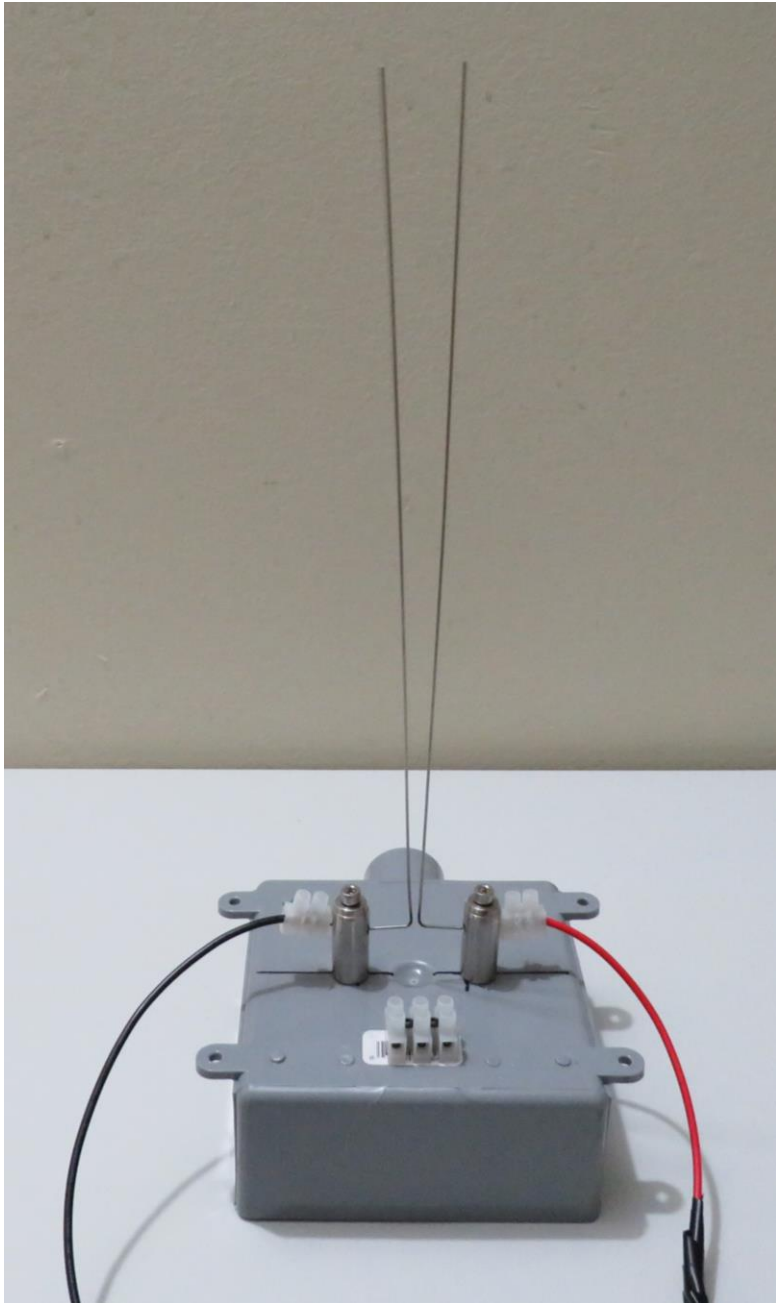


Photo and Video-link of the Tesla coil Connected to the Jacob's Ladder

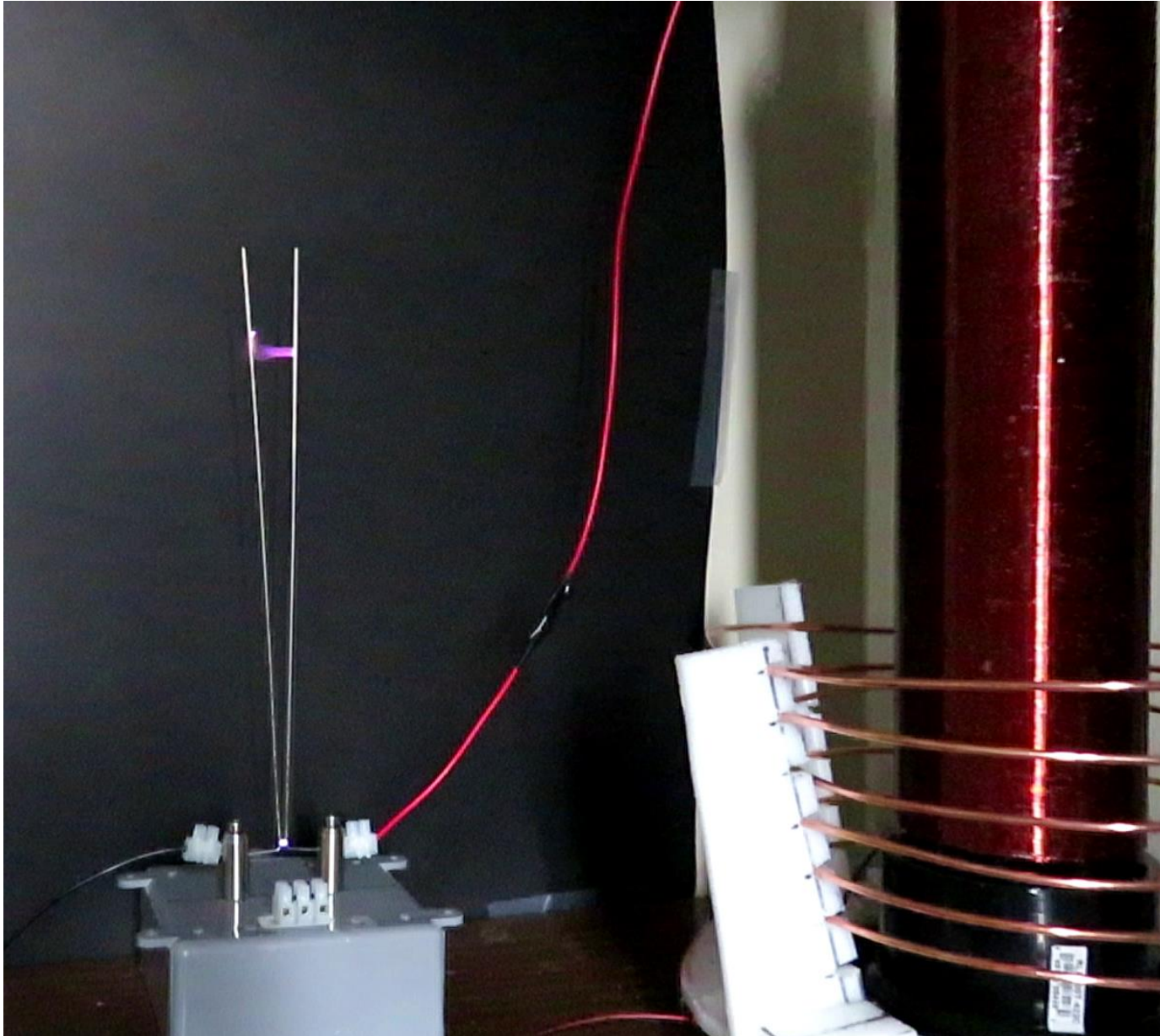


<https://www.youtube.com/watch?v=ZHksr7DKXZ4&feature=youtu.be>

Tesla coil without the Top Load

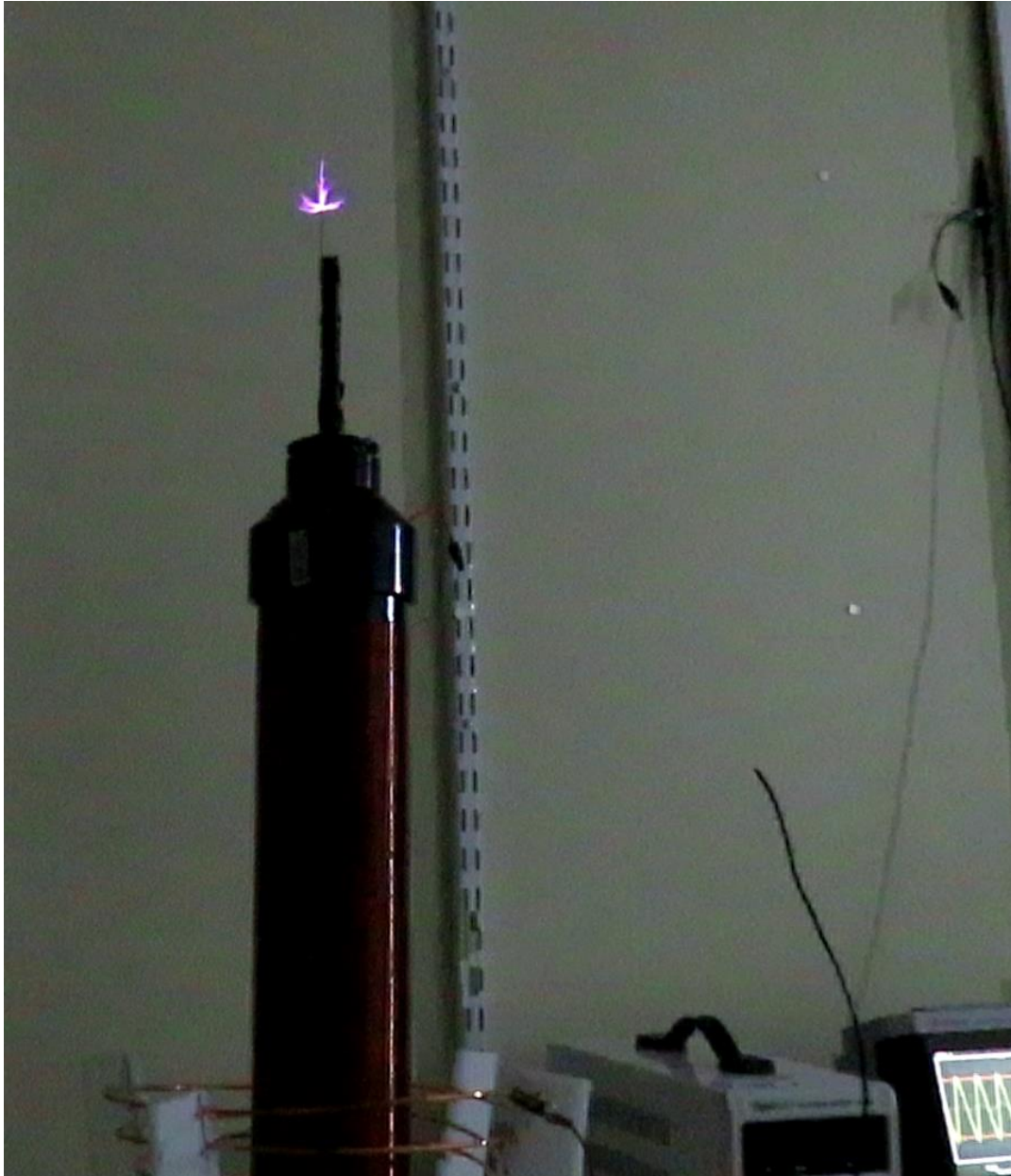


<https://www.youtube.com/watch?v=nxPptbAT3AE&feature=youtu.be>

Manually Tuned Tesla Coil Driver

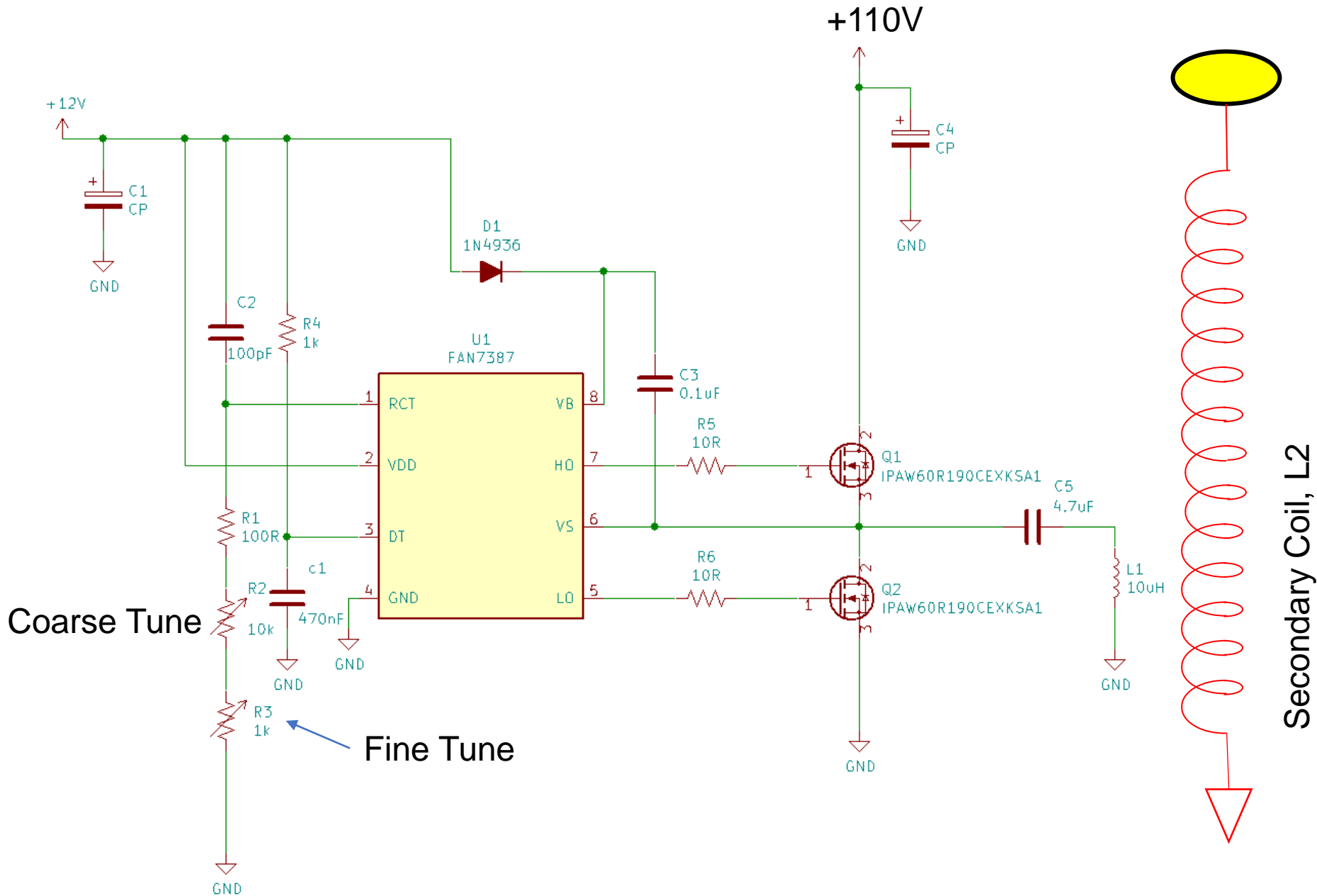

Practical Half-Bridge Driver

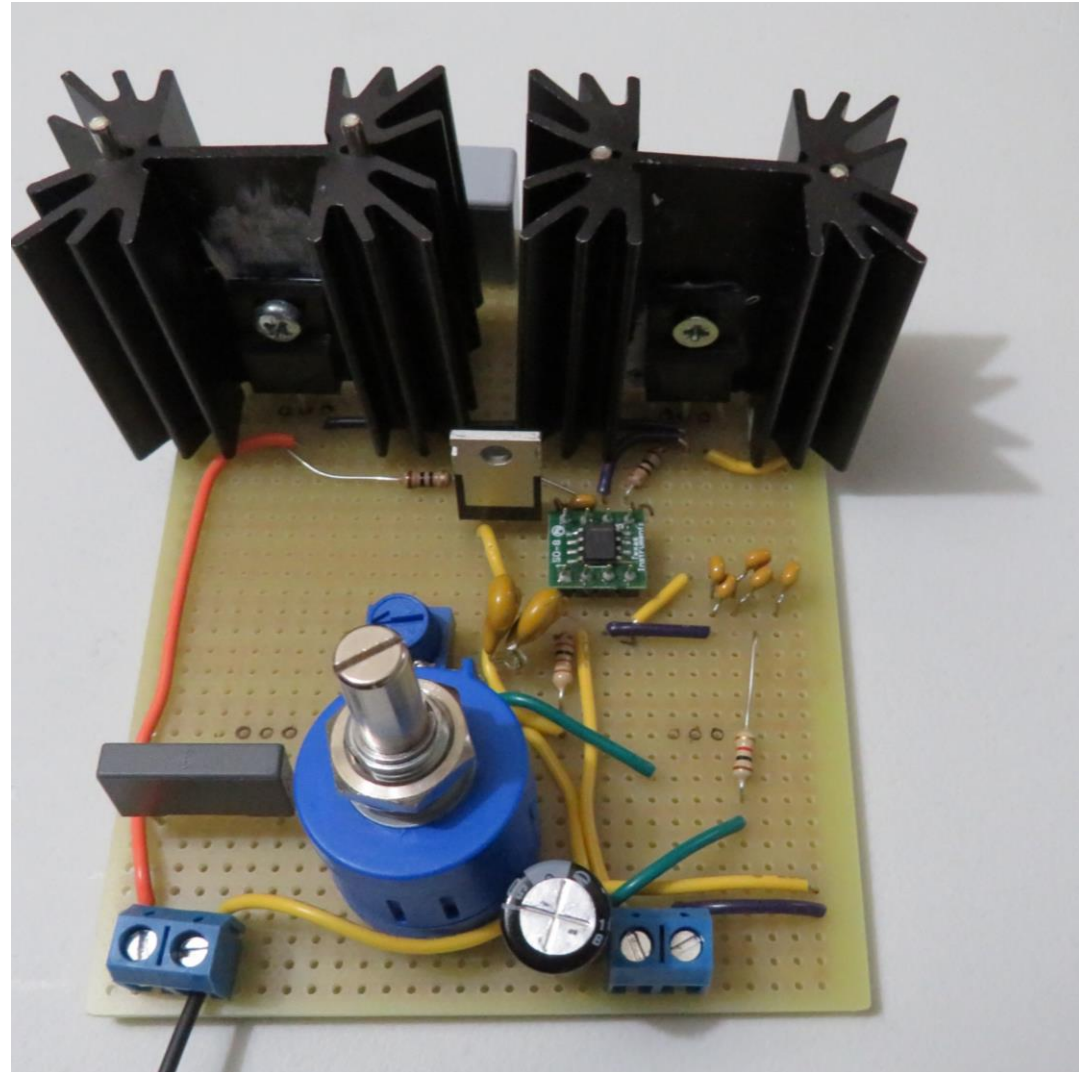Using this half-bridge driver circuit shows similar kind of effect as that of the class-E Slayer exciter circuit. However, difficult to tune. Tuning is achieved by two knobs: coarse and finetuning



Reference

Best: lot of workable practical examples

<https://www.stevhv.4hv.org/SSTCindex.htm>